

# **DEPARTMENT OF ELECTRONICS ENGINEERING**

**Programme: UG - B.Tech**

**Electronics Devices and Circuits Lab  
(ECC210)**

**Laboratory Manual**



**INDIAN INSTITUTE OF TECHNOLOGY(ISM),  
DHANBAD  
JHARKHAND - 826004**

## LIST OF EXPERIMENTS

<b>Exp. No.</b>	<b>Title</b>	<b>Page no.</b>
1	Design of OPAMP based circuit for performing various mathematical operation (Part I)	3-8
2	Design of OPAMP based circuit for performing various mathematical operation (Part II)	9-18
3	Design and performance analysis of various active filters	19-25
4	Generation of different waveforms using OPAMP (Part I)	26-32
5	Generation of different waveforms using OPAMP (Part II)	33-38
6	Design a Common Emitter amplifier with proper Q-point setting and study the frequency response of the amplifier	39-44
7	Performance analysis (Frequency response) of cascaded amplifiers	45-50
8	Drain and Transfer characteristic of field effect transistor (FET)	51-55
9	Realization of Current Mirror circuit	56-59
10	Design and study of input (Differential pair) and output (Darlington) stage of OPAMP	60-63

## **EXPERIMENT -01**

### DESIGN OF OPAMP BASED CIRCUIT FOR PERFORMING VARIOUS MATHEMATICAL OPERATION (PART I).

#### **OBJECTIVE:**

After completion of this experiment, student will be able to design and setup an inverting amplifier, non- inverting amplifier and voltage follower/ buffer using OP- AMP.

#### **APPARATUS AND COMPONENTS REQUIRED:**

1. Dual power supply +/- 15V
2. DC power source
3. Function generator (0-1MHz)
4. Oscilloscope
5. Bread board (For Hardware) / Multisim Software (Software)
6. IC 741C
7. Resistor
8. Probes and connecting wires

#### **THEORY AND EXPLANATION:**

##### **1. INVERTING AMPLIFIER**

An inverting amplifier using op-amp is a type of amplifier where the output waveform will be 180° out of phase to the input waveform. The input waveform will be amplified by the factor  $A_v$  (voltage gain of the amplifier) in magnitude and its phase will be inverted. In the inverting amplifier circuit, the signal to be amplified is applied to the inverting input of the op-amp through the input resistance  $R_1$ .  $R_f$  is the feedback resistor.  $R_f$  and  $R_1$  together determine the gain of the amplifier. Inverting operational amplifier gain can be expressed using the equation  $A_F = -R_F/R_1$ . Negative sign implies that the output signal is out of phase.

At the node  $v_2$ , we have  $i_{in} = i_F + i_{B2}$ . Since  $R_i$  is very large, the bias current is negligibly small and we can write  $i_{in} \cong i_F$

$$\text{Or, } \frac{v_{in} - v_2}{R_1} = \frac{v_2 - v_o}{R_F}.$$

$$\text{Again, } v_1 - v_2 = v_o/A.$$

Since  $v_1 = 0$ , we get  $v_2 = -v_o/A$ .

Therefore,

$$\frac{v_{in} + (v_o/A)}{R_1} = \frac{-(v_o/A) - v_o}{R_F}$$

Or, 
$$A_F = \frac{v_o}{v_{in}} = -\frac{AR_F}{R_1 + R_F + AR_1}$$

Since the internal gain of the OPAMP ( $A$ ) is very high we can assume  $AR_1 \gg R_1 + R_F$  and  $A_F = -R_F/R_1$ . The negative sign indicates that the input and output signals are  $180^\circ$  out of phase. Further if  $R_1 = R_F$  the output signal is equal in amplitude but opposite in phase to that of input signal. This circuit represents an inverter.

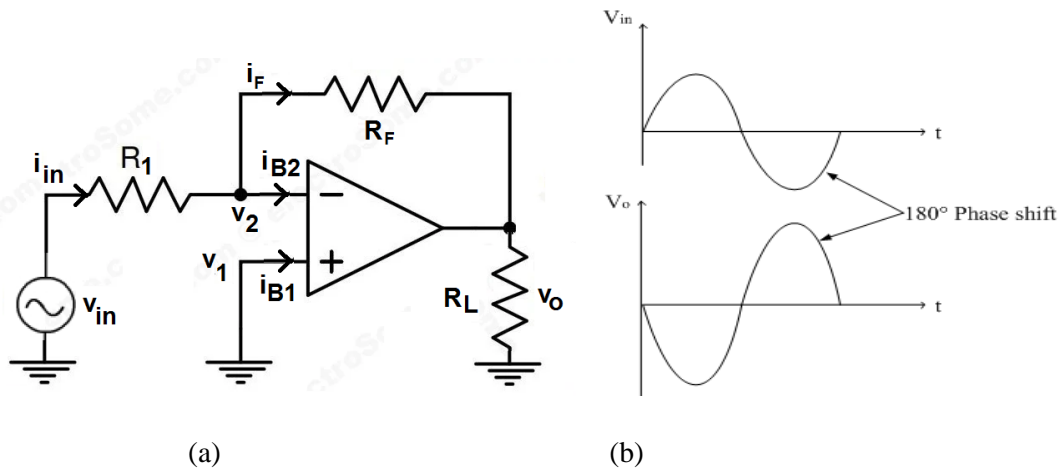


Fig.1.1. (a) Circuit diagram, (b) Input and output Waveform of inverting amplifier

This means that if we replace the  $v_{in}$  and  $R_1$  combination by a current source  $i_{in}$ , as shown Fig. 1.2, the output voltage  $v_o$  becomes proportional to the input voltage. In other words the figure represents a current to voltage converter that converts the input current into a proportional output voltage.

 


Fig. 1.2 Current to Voltage Converter

## II. NON- INVERTING AMPLIFIER

A non-inverting amplifier is an op-amp circuit configuration which produces an amplified output signal is shown in Fig 1.3. This output signal of non-inverting OPAMP is in-phase with the input signal applied.

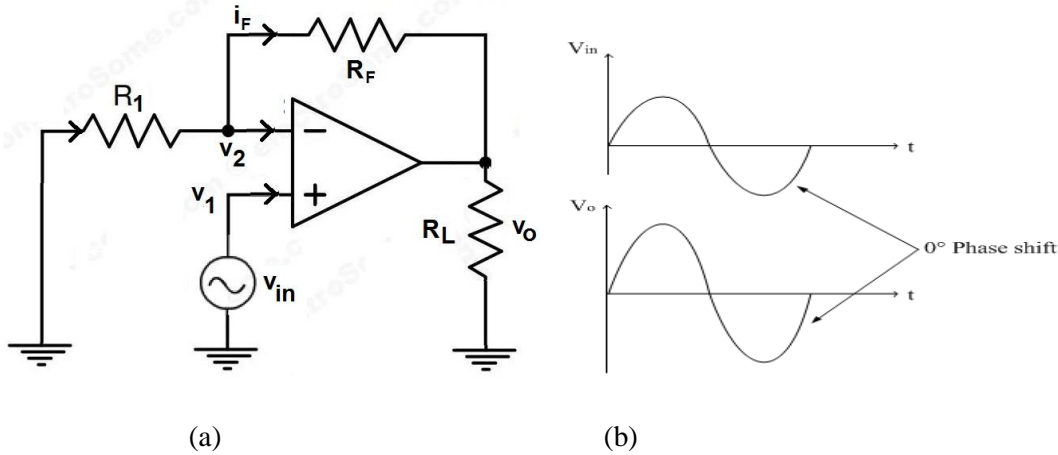


Fig.1.3. (a) Circuit diagram, (b) Input and output Waveform of non- inverting amplifier

At the input loop,  $v_{id} = v_{in} - v_f$ .

The closed loop gain is  $A_F = v_o/v_{in}$ .

Again,  $v_o = A(v_1 - v_2)$ .

Now,  $v_1 = v_{in}$  and  $v_2 = v_f = \frac{R_1}{R_1 + R_F} v_o$  (assuming  $R_i \gg R_1$ ).

Therefore,  $v_o = A \left( v_{in} - \frac{R_1 v_o}{R_1 + R_F} \right)$

Or,  $v_o = \frac{A(R_1 + R_F) v_{in}}{R_1 + R_F + AR_1}$ .

Thus,  $A_F = \frac{v_o}{v_{in}} = \frac{A(R_1 + R_F)}{R_1 + R_F + AR_1}$ .

Since A is very large, we can assume  $AR_1 \gg R_1 + R_F$  and therefore  $A_F = 1 + \frac{R_F}{R_1}$ .

If we open the resistance  $R_1$  and short the resistance  $R_F$ , as shown in Fig. 1.4, then the gain of the non-inverting amplifier becomes lowest and equal to one. Such circuit is called a voltage follower because the output voltage is equal and in phase with the input. In other words the output follows the input. It is similar to the discrete emitter follower, but the voltage follower is preferred over

emitter follower as it has much higher input resistance and the output amplitude is exactly equal to the input.

 


Fig. 1.4. Voltage Follower Circuit

**PROCEDURE:**

1. Derive / Check the component values [Typical values of resistors are in  $k\Omega$ ].
2. Setup the circuit on the breadboard / Multisim software and check the connections (for software simulation).
3. Apply suitable ac voltage levels and waveforms at the input terminal. [Typical values 1-2 Vpp, Frequency = 1 kHz, Waveform: Sinusoidal, dc / ac for voltage follower]
4. Observe input and output on two channels of the oscilloscope simultaneously. Note down and draw the input and output waveforms on the graph.
5. Compare the practical values with theoretical values.
6. For the frequency response of the inverting and non- inverting amplifier, vary the frequency of the input waveform and enter into the tabular column. Also plot the frequency curve.
7. For voltage follower circuit, feed a waveform to the input and note down the output amplitude by varying the input amplitude of the waveform. Enter it in the tabular column.

**OBSERVATION TABLE:**

**TABLE - 1: FOR INVERTING / NON-INVERTING AMPLIFIER**

$R_1$ ( $k\Omega$ )	$R_f$ ( $k\Omega$ )	$V_{in}$ (Volt)	$V_o$ (Volt)	Theoretical Gain	Practical Gain (dB)

**TABLE - 2: FOR FREQUENCY RESPONSE OF THE INVERTING / NON- INVERTING AMPLIFIER**

Frequency (Hz - kHz)	$V_0$ (V)	Gain	Gain(dB)

**TABLE - 3: FOR VOLTAGE FOLLOWER**

Input	Output		Input	Output	
$V_{in}$ (dc)	Theoretical	Practical	$V_{in}$ (ac)	Theoretical	Practical

**OBJERVATIONS:**

Explain your result here.

**CONCLUSION:**

Various mathematical operation of OPAMP such inverting, non- inverting amplifier and voltage buffer has been studied.

**PROBLEMS:**

1. Design an inverting op-amp circuit for which the gain is  $-5V/V$  and the total resistance used is 120 kohm.
2. Calculate the output voltage of a non- inverting amplifier for values of  $V_1 = 2V$ ,  $R_f = 500$  kohm and  $R_1 = 100$  kohm
3. An op-amp with an open loop gain of  $100V/V$  is used in the inverting configuration. If in this application the output voltages range from  $-10V$  to  $+10V$ , what is the maximum voltage by which the virtual ground node departs from its ideal value.
4. What is the typical conditions of non- inverting amplifier to operate in linear region?

**TYPICAL QUESTIONS:**

1. In what way the voltage follower is the special case of non-inverting amplifier and current-to-voltage converter is the special case of inverting amplifier?
2. What kind of feedback is present in inverting /non- inverting amplifier?
3. What is virtual ground? What happens when the inverting / non-inverting is not grounded in case of non-inverting / inverting amplifier?
4. Describe different pin configurations of IC741C.

5. How to design an inverting / non-inverting amplifier for a specified gain?
6. How the feed-back effects the input and output resistance of an inverting / non-inverting amplifier as compared to an open loop OPAMP?
7. How the feed-back effects the gain and bandwidth of an inverting / non-inverting amplifier as compared to an open loop OPAMP?
8. What are the general assumptions that we make during the design of an OPAMP feedback circuit.
9. What are the characteristics of an ideal and a practical OPAMP?
10. Define different parameters (such as input offset voltage, input offset current, input bias current, slew rate, CMRR etc.) related to OPAMP.



## **EXPERIMENT -2**

### DESIGN OF OPAMP BASED CIRCUIT FOR PERFORMING VARIOUS MATHEMATICAL OPERATION (PART II).

#### **OBJECTIVE:**

After completion of this experiment, student will be able to design and setup a summing amplifier, difference amplifier, integrator, differentiator using OPAMP.

#### **APPARATUS AND COMPONENTS REQUIRED:**

1. Dual power supply +/- 15V
2. DC power source
3. Function generator (0-1MHz)
4. Oscilloscope
5. Bread board (For Hardware) / Multisim Software (Software)
6. IC 741C
7. Resistor
8. Capacitor
9. Probes and connecting wires

#### **THEORY AND EXPLANATION**

##### **1. ADDER**

OPAMP can be used to design a circuit whose output is the sum of two or more input signals. Such a circuit is called a summing amplifier or an adder. Summing amplifier can be classified as inverting & non-inverting summer depending on the input applied to inverting & non-inverting terminals respectively. Circuit diagram Fig.2.1 (a) shows an N-input inverting summing amplifier whereas circuit diagram 2.1 (a) shows an N-input non-inverting summing amplifier. For inverting summing amplifier the output will be amplified version of the sum of the N input voltages with  $180^{\circ}$  phase reversal whereas for non-inverting summing amplifier the output will be amplified version of the sum of the N input voltages with  $0^{\circ}$  phase difference.

*N-input inverting summing amplifier:*

$$i_{in} = i_1 + i_2 + \dots + i_N \cong i_F$$

$$\text{Or, } \frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \dots + \frac{v_N - 0}{R_N} = \frac{0 - v_0}{R_F}$$

$$\text{Or, } \frac{v_1}{R_1} + \frac{v_2}{R_2} + \dots + \frac{v_N}{R_N} = -\frac{v_0}{R_F}$$

$$\text{Or, } v_0 = -R_F \left( \frac{v_1}{R_1} + \frac{v_2}{R_2} + \dots + \frac{v_N}{R_N} \right)$$

Such amplifier is called scaling or weighted amplifier as each input voltage is amplified by a different factor. If  $R_1 = R_2 = \dots = R_N = R$  then  $v_0 = -R_F (v_1 + v_2 + \dots + v_N)/R$ . If  $R_F/R = 1/N$  then  $v_0 = -(v_1 + v_2 + \dots + v_N)/N$ . Therefore the output is the average of the input voltages. Further if  $R_F = R$  then  $v_0 = -(v_1 + v_2 + \dots + v_N)$ . Thus output is the algebraic sum of the input voltages.

*N-input non-inverting summing amplifier:*

Using superposition principle at node  $V_1$  we can write

$$V_1 = \frac{R/2}{R + R/2} V_a + \frac{R/2}{R + R/2} V_b + \frac{R/2}{R + R/2} V_c$$

$$\text{Or, } V_1 = (V_a + V_b + V_c)/3$$

$$\text{Now, } \frac{0 - V_2}{R_1} = \frac{V_2 - V_o}{R_F}$$


$$\text{Or, } \frac{V_o}{R_F} = \frac{V_2}{R_F} + \frac{V_2}{R_1} = V_2 \left( \frac{R_1 + R_F}{R_1 R_F} \right)$$

$$\text{Or, } V_o = V_2 \left( \frac{R_1 + R_F}{R_1} \right) = V_2 \left( 1 + \frac{R_F}{R_1} \right)$$


$$\text{Since } V_2 = V_1 \text{ we can write, } V_o = \left( 1 + \frac{R_F}{R_1} \right) \frac{V_a + V_b + V_c}{3}$$

Above equation implies that output voltage is average of the input voltage times the gain of the circuit  $1 + \frac{R_F}{R_1}$ . Such amplifier is known as averaging amplifier. To get the actual average  $R_F$  should be zero and

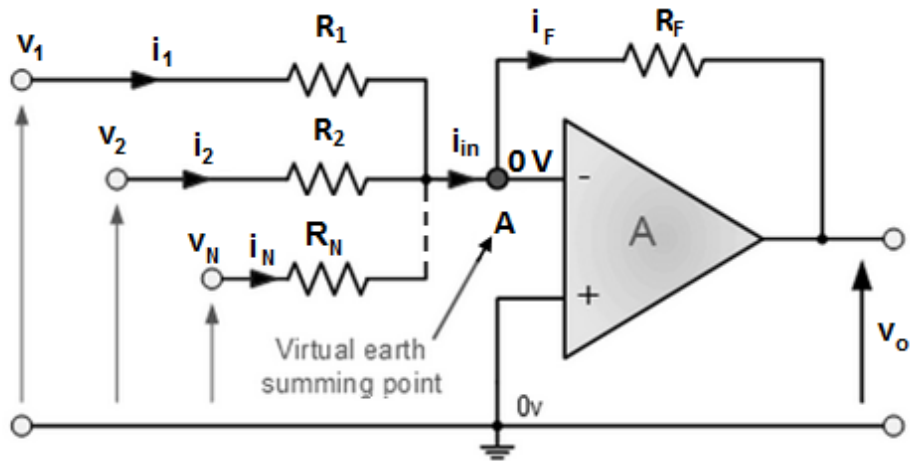$R_1$  should be opened. To get summed output  $1 + \frac{R_F}{R_1}$  should be equal to 3 or  $R_F$  should be equal to  $2R_1$ .



(a)

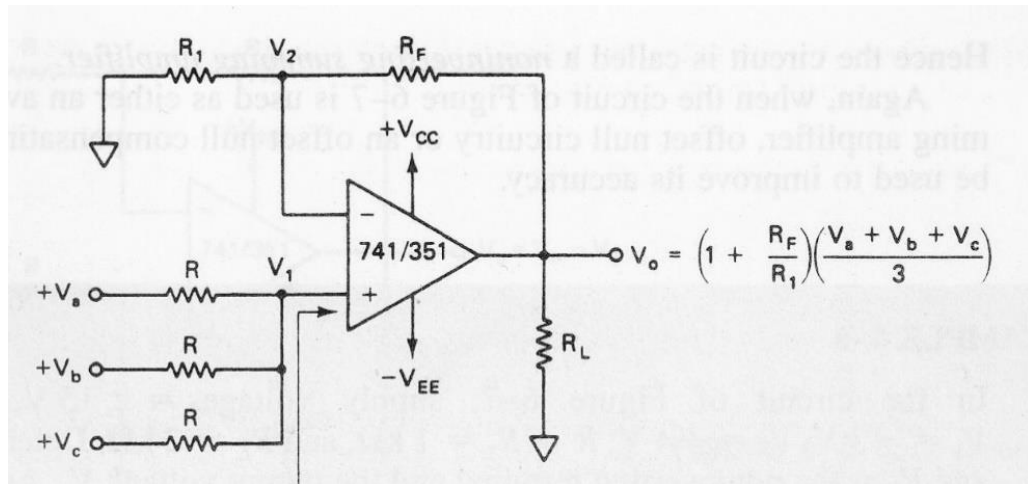

(b)

Fig.2.1. Circuit diagram of adder (a) Inverting summing amplifier, (b) Non-inverting summing amplifier

## 2. SUBTRACTOR

A difference or subtractor amplifier is a circuit that gives the amplified version of the difference of the two inputs. An OPAMP differential amplifier is shown in circuit diagram Fig.2.2.

At node  $v_x$  we can write,  $\frac{v_1 - v_x}{R_1} = \frac{v_x - v_o}{R_2}$

Since  $v_x = v_y$  at node  $v_y$  we can write,  $\frac{v_2 - v_x}{R_1} = \frac{v_x - 0}{R_2}$ .

Subtracting the former equation from the later, we get  $\frac{v_2 - v_x - v_1 + v_x}{R_1} = \frac{v_x - v_x + v_o}{R_2}$

Or,  $v_o = R_2(v_2 - v_1)/R_1$ .

Above equation implies that output voltage is difference of the input voltage times the gain of the circuit  $R_2/R_1$ . Such amplifier is known as difference amplifier.

To get actual difference output (or subtraction)  $R_2/R_1$  should be equal to 1 or  $R_2$  should be equal to  $R_1$ .

 


Fig.2.2. Circuit diagram for subtractor.

### 3. INTEGRATOR


It is a closed loop op-amp circuit which performs the mathematical operation of integration. That is the output waveform is the integral of the input voltage. This circuit also works as low pass filter. The integrator circuit is constructed from basic inverting amplifier by replacing the feedback resistance with a capacitor, as shown in circuit diagram 2.3. Since the non-inverting terminal is at ground potential we can assume the node  $v_2$  is at ground potential.

From the circuit we can write  $\frac{v_{in} - 0}{R_1} = C_F \frac{d}{dt}(0 - v_o)$


Or,  $\frac{v_{in}}{R_1} = -C_F \frac{dv_o}{dt}$ .

Or,  $v_o = -\frac{1}{R_1 C_F} \int_0^t v_{in} dt + C$

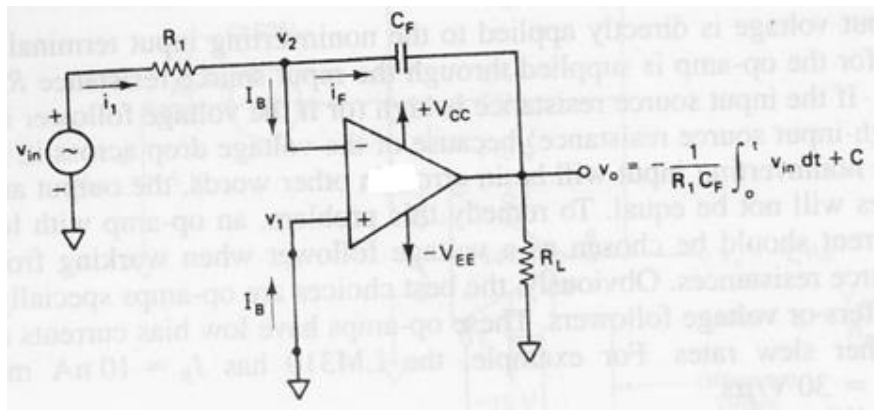where “C” is the integration constant and is proportional to the value of output voltage  $v_o$  at time  $t = 0$ .



(a)

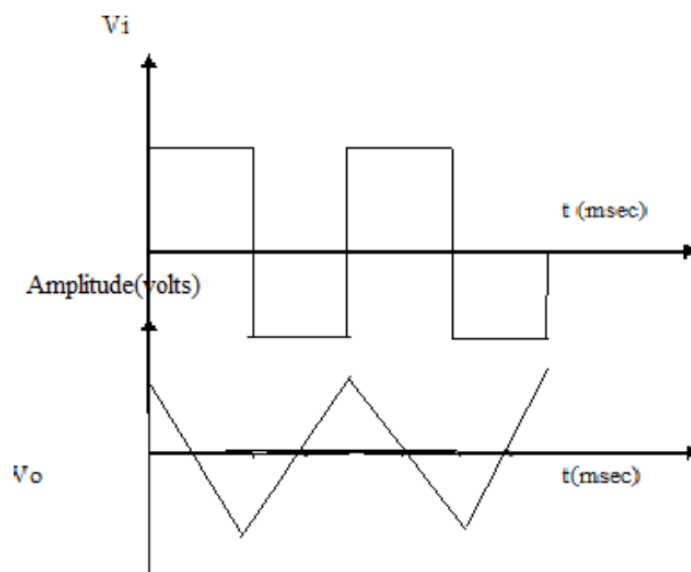

(b)

Fig.2.4. (a) Circuit diagram for integrator and (b) its input and output waveform

When  $v_{in} = 0$  the integrator works as an open-loop amplifier, because the capacitor acts as an open circuit to the input offset voltage  $V_{io}$ . Therefore a practical integrator uses a resistor  $R_F$  across  $C_F$ , as shown in circuit diagram 2.4. The  $R_F$  limits the low frequency gain and hence minimizes the variations in the output voltage.

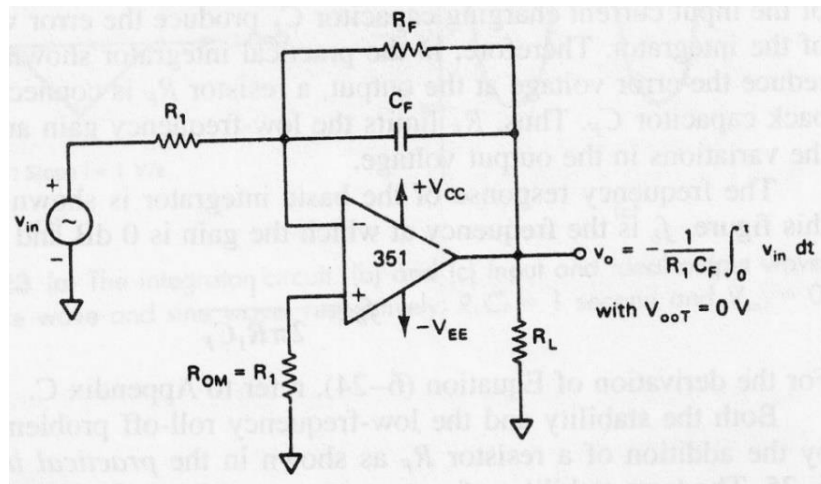


Fig. 2.4. Practical integrator

## 5. DIFFERENTIATOR

It is an OPAMP circuit which performs the mathematical operation of differentiation. That is the output waveform is the derivative or differential of the input voltage. This circuit also works as high pass filter. The differentiator circuit is constructed from basic inverting amplifier by replacing the input resistance with a capacitor, as shown in circuit diagram 2.5. Since the non-inverting terminal is at ground potential we can assume the node  $v_2$  is at ground potential.


From the circuit we can write

$$C_1 \frac{d}{dt}(v_{in} - 0) = \frac{0 - v_o}{R_F}$$


$$\text{Or, } v_o = -R_F C_1 \frac{dv_{in}}{dt}.$$

Above equation implies the output voltage is  $C_F R_1$  times the negative instantaneous rate of change of  $v_{in}$  with time. Therefore a cosine input will produce a sine wave output, or a triangular input will produce a square wave output

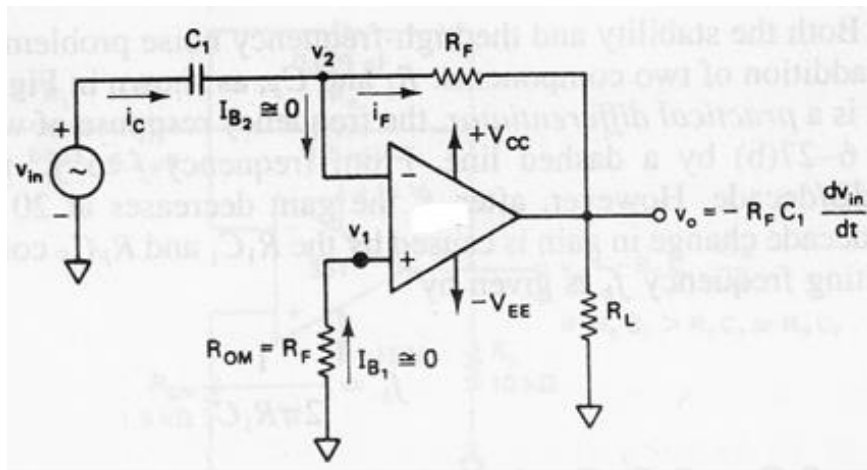When  $v_{in} = 0$  the differentiator works as an open-loop amplifier, because the capacitor acts as an open circuit to the input offset voltage  $V_{io}$ . Therefore a practical differentiator uses a series resistor with the capacitor.



(a)

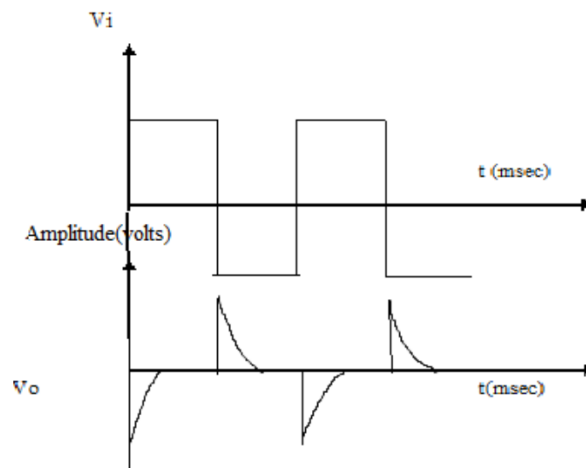

(b)

Fig.2.5. (a) Circuit diagram for differentiator and (b) its input and output waveform.

**PROCEDURE:**

1. Derive / Check the component values [Typical values of resistors are in  $k\Omega$  and capacitors in  $\mu F$ . The feedback resistor in circuit diagram 2.4 should be very high as compared to other resistors].
2. Setup the circuit on the breadboard / Multisim software and check the connections (for software simulation).
3. Apply suitable voltage levels and waveforms (DC + DC /DC + ac /ac + ac / ac) at the input terminal(s). [Typical values DC: 1 – 2 V, ac: 1-2 V pp, Frequency = 1 kHz, Waveform: Sinusoidal for adder and subtractor, square wave for integrator and differentiator]
4. Observe input and output on two channels of the oscilloscope simultaneously. Note down and draw the input and output waveforms on the graph.
5. Compare the practical values with theoretical values.

6. For integrator / differentiator feed a waveform to the input and note down the output amplitude by varying the frequency of the waveform. Enter it in the tabular column and plot the frequency curve. [Typical waveform: square wave, Frequency: From few Hz to few kHz]

**OBSERVATION TABLE:**

**TABLE -1: FOR ADDER / SUBTRACTOR CIRCUIT**

Input		Output		Input		Output		Input		output	
V1(dc)	V2(dc)	Theoretical	Practical	V1(dc)	V2(ac)	Theoretical	Practical	V1(ac)	V2(ac)	Theoretical	Practical

**TABLE- 2: FOR INTEGRATOR/ DIFFERENTIATOR**

Type	Input waveform	Output waveform	Output voltage(theoretical)	Output voltage(practical)	% error
Differentiator /Integrator					

**TABLE- 3: FOR INTEGRATOR/ DIFFERENTIATION**

Frequency	V <sub>in</sub> (Volt)	V <sub>o</sub> (Volt)	Gain (dB)

**OBSERVATIONS:**

Explain your result here.



## **CONCLUSION:**

Various mathematical operation of OPAMP such as adder, subtractor, integrator and differentiator has been studied. The realization of differentiation act as high pass filter and integration act as low pass filter also has been studied.

## **PROBLEMS:**

1. Design a circuit using OPAMP to add 3/4 numbers.
2. Design a circuit using OPAMP to perform  $5 - 3 = 2$
3. Design a circuit using OPAMP to perform integration of a square wave of PRF 1 KHz
4. Design a circuit using OPAMP to perform differentiation of a square wave of PRF 1 KHz/2 KHz/3KHz

## **TYPICAL QUESTIONS:**

1. What happens to the accuracy of integration as the input frequency is increased?
2. At very low frequencies, does the integrator behave more like a true integrator, or like an amplifier?
3. What is the purpose of the feedback resistor in circuit diagram 2.4?
4. What happens to the accuracy of differentiation as the input frequency is decreased?
5. At very high frequencies, does the differentiator behave more like a true differentiator, or like an amplifier?
6. What is the purpose of the series resistor in circuit diagram 2.5?
7. How can you design an average amplifier?
8. What are the general assumptions that we make during the design of an OPAMP feedback circuit.
9. What are the characteristics of an ideal and a practical OPAMP?
10. Define different parameters (such as input offset voltage, input offset current, input bias current, slew rate, CMRR etc.) related to OPAMP.

### **OTHER RELATED OPAMP CIRCUIT DESIGN:**

1. Summing amplifier using differential configuration
2. Instrumentation amplifier
3. Differential input and differential output amplifier
4. Voltage to current converter
5. Logarithmic Amplifier
6. Anti-logarithmic amplifier.

## **EXPERIMENT -03**

### **DESIGN AND PERFORMANCE ANALYSIS OF VARIOUS ACTIVE FILTERS.**

#### **OBJECTIVE:**

After completion of this experiment, student will be able to design 1<sup>st</sup> order and 2<sup>nd</sup> order low pass filter and high pass filter by using Op-Amp.

#### **APPARATUS AND COMPONENTS REQUIRED:**

1. Dual power supply +/- 15V
2. DC power source
3. Function generator
4. Oscilloscope
5. Bread board (For Hardware) / Multisim Software (Software)
6. IC 741C
7. Resistor (Order: k $\Omega$ )
8. Capacitors (Order:  $\mu$ F)
9. Probes and connecting wires

#### **THEORY AND EXPLANATION:**

##### **1. LOW PASS FILTER**

It is a network that allows the flow of signal with frequency below the cut-off frequency,  $f_H$ , and blocks the signals with frequency above the cut-off frequency. Here, few active low pass filters are realized by using Op-amp. Active low pass filters have the same principle of operation and frequency response as passive low pass filter, the only difference is that it uses an op-amp for amplification and gain control. The simplest form of an active low pass filter is a passive low pass filter connected at the input of an inverting /non-inverting amplifier.

*First-order low-pass Butterworth filter:*

Schematic diagram of a first –order low-pass Butterworth filter is shown below.

 


Fig. 3.1. Circuit diagram of a First-order low-pass filter.

The OPAMP is used in the non-inverting condition; hence it does not load down the RC network. The voltage at the non-inverting terminal is

$$v_1 = \frac{1}{R + \frac{1}{j2\pi fC}} v_{in} = \frac{v_{in}}{1 + j2\pi fCR}$$

The output voltage is

$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_1 = \left(1 + \frac{R_F}{R_1}\right) \frac{v_{in}}{1 + j2\pi fCR}$$

$$\text{Or, } v_o = \frac{A_f}{1 + j(f/f_H)} v_{in}$$

where  $A_F$  is the pass band gain of the filter and  $f_H$  is high cut-off frequency of the filter.

$$\left|\frac{v_o}{v_{in}}\right| = \frac{A_f}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \text{ and } \varphi = \tan^{-1}(f/f_H).$$

For,  $f < f_H$ ,  $\left|\frac{v_o}{v_{in}}\right| \cong A_F$ ; at  $f = f_H$   $\left|\frac{v_o}{v_{in}}\right| \cong \frac{A_F}{\sqrt{2}} = 0.707A_F$ , at  $f > f_H$   $\left|\frac{v_o}{v_{in}}\right| < A_F$ .

In designing low-pass active filter the value of C is generally taken less than 1  $\mu\text{F}$ . First –order low-pass Butterworth filter provides a 20 dB/decade roll-off. To get 40 dB/decade roll-off a second –order low-pass Butterworth filter should be used.

*Second-order low-pass Butterworth filter:*

Schematic diagram of a second –order low-pas Butterworth filter is shown in circuit diagram 3.2.

 


Fig.3.2 Circuit diagram of a second-order low-pass filter.

The cut-off frequency is

$$f_H = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

The gain of the filter is

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_f}{\sqrt{1 + (f/f_H)^4}}$$

To design a second –order low-pas Butterworth filter we generally choose  $R_2 = R_3 = R$ ,  $C_2 = C_3 = C$  and  $C \leq 1\mu\text{F}$ . Therefore,

$$f_H = \frac{1}{2\pi RC}$$

To get a Butterworth response the gain of the filter should be equal to 1.586. Therefore

$$1 + \frac{R_F}{R_1} = 1.586$$

$$\text{Or, } R_F = 0.586 R_1$$

Higher order low-pass filters, such as third order, fourth-order low-pass filters are formed simply using cascaded first and / or second order low-pass filters.

## 2. HIGH PASS FILTER

It is a network that allows the flow of signal with frequency above the cut-off frequency,  $f_L$ , and blocks the signals with frequency below the cut-off frequency. Here, few active high pass filters are realized by using Op-amp. Active high pass filters have the same principle of operation and frequency response as passive high pass filter, the only difference is that it uses an op-amp for amplification and gain control. The simplest form of an active high pass filter is a passive high pass filter connected at the input of an inverting /non-inverting amplifier.

Schematic diagrams of a first-order high-pass Butterworth filter are shown in circuit diagram 3.3 and 3.4, respectively. The filters can be achieved by interchanging the positions of the capacitors and resistors of a first-order and a second-order low pass Butterworth filter, respectively.

For the first order high pass Butterworth filter we have

$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_1 = \left(1 + \frac{R_F}{R_1}\right) \frac{j2\pi fCR}{1+j2\pi fCR} v_{in}$$

$$\text{Or, } v_o = A_F \frac{j(f/f_L)}{1+j(f/f_L)} v_{in}$$

where  $A_F$  is the passband gain of the filter and  $f_L$  is low cutoff frequency of the filter. The gain of the first –order high-pass Butterworth filter is

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_f(f/f_L)}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}}$$

Similarly, the gain of the second–order high-pass Butterworth filter is,

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_f(f/f_L)}{\sqrt{1 + \left(\frac{f}{f_L}\right)^4}}$$

 


Fig.3.3 Circuit diagram of a first-order high pass Butterworth filter

 


Fig.3.4 Circuit diagram of second-order high pass Butterworth filter

## PROCEDURE

3. Derive / Check the component values [Typical values of resistors are in  $k\Omega$ ].
4. Setup the circuit on the breadboard / Multisim software and check the connections (for software simulation).
5. Apply suitable ac voltage levels and waveforms at the input terminal. [Typical values 1-2 V pp, Waveform: Sinusoidal.
6. For the frequency response of the low pass and high pass filters, vary the frequency of the input waveform and enter into the tabular column. Also plot the frequency curve.

## OBSERVATION TABLE

**TABLE - 1:** FOR 1<sup>ST</sup> ORDER LOW PASS / 2<sup>ND</sup> ORDER LOW PASS / 1<sup>ST</sup> ORDER HIGH PASS / 2<sup>ND</sup> ORDER HIGH PASS FILTERS

Frequency (in Hz)	Input Voltage, $V_i$	Output Voltage, $V_o$	Gain (in dB)

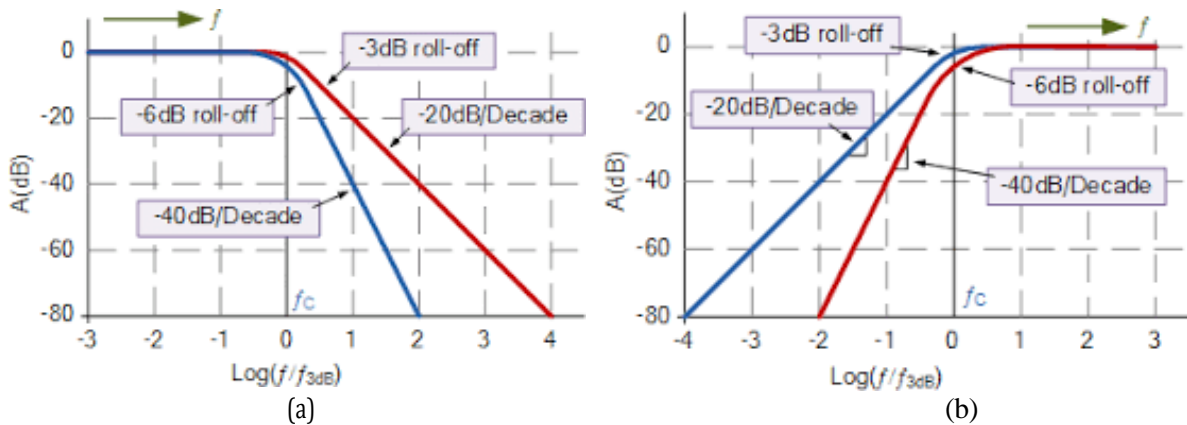


Fig. 3.5. Expected frequency Responses of (a) 1<sup>st</sup> and 2<sup>nd</sup> order low pass filter and (b) 1<sup>st</sup> and 2<sup>nd</sup> order high pass filter

## OBJERVATIONS

Explain your result here.

## CONCLUSION

1<sup>st</sup> and 2<sup>nd</sup> order active low pass and high pass filters have been design using OPAMP and there frequency responses have been studied.

## TYPICAL QUESTIONS

1. Describe different pin configurations of IC741C.
2. What is the gain bandwidth product of OPAMP?
3. What are the general assumptions that we make during the design of an active filter using an OPAMP?
4. What are the characteristics of an ideal filter and a practical filter?
5. What is roll-off rate in filter design?



6. Design a 1<sup>st</sup> order and 2<sup>nd</sup> order HPF and LPF using op-amp circuit for cut-off frequency 5 kHz with Gain=2.
7. Design a 3<sup>rd</sup> order HPF and LPF using op-amp circuit for cut-off frequency 5 kHz with Gain=2.
8. How can you design higher order active low pass and high pass filters using the knowledge you gathered during the experiment?
9. How can you design a wide band active band pass filter using the knowledge you gathered during the experiment?
10. How can you design a wide band active band stop filter using the knowledge you gathered during the experiment?

## **OTHER RELATED OPAMP CIRCUIT DESIGN**

1. Design of a third order and a fourth order active low pass filter using first order and / or second order active low pass filters.
2. Design of a third order and a fourth order active high pass filter using first order and / or second order active high pass filters.
3. Design of a first-order active wide-band band pass filter using a first order active low pass and a first order active high pass filters.
4. Design of an active narrow-band band pass filter using a single op amp.
5. Design of a first-order active wide-band band stop filter using a first order active low pass filter, a first order active high pass filter, and an adder circuit.
6. Design of an active narrow-band band stop filter using a single op amp.
7. Design of an active all pass filter using a single op amp.

## EXPERIMENT – 04

### GENERATION OF DIFFERENT WAVEFORMS USING OPAMP (Part I)

#### OBJECTIVE:

After completion of this experiment, student will be able to design OPAMP Comparator, Zero-Crossing detector, and Schmitt trigger Circuits.

#### APPARATUS AND COMPONENTS REQUIRED:

1. Dual power supply +/- 15 V
2. DC power source
3. Function Generator
4. Oscilloscope
5. Bread board (for hardware) / Multisim Software (Software)
6. IC 741C
7. Resistors
8. Capacitors
9. Probes and connecting wires

#### THEORY AND EXPLANATION

##### 1. OPAMP Comparator

A comparator circuit compares a signal voltage applied at one input of an OPAMP with a known reference voltage at the other input. It is basically an open loop OPAMP with output  $\pm V_{SAT}$ . It is also called a voltage level detector because for the desired value of  $v_{ref}$ , the voltage level at the input can be detected. In general, comparators can be two types – non-inverting and inverting. The schematic diagram of a non-inverting comparator is shown in Fig. 4.1, where the input signal is fed at the non-inverting terminal of the OPAMP. In practical comparator circuit  $v_{ref}$  is obtained using a 10 k $\Omega$  potentiometer. When  $v_{in} < V_{ref}$ , the output voltage is at  $-V_{SAT}$  because the voltage at inverting input is higher than at non-inverting input. When  $v_{in} > V_{ref}$ , the output voltage is at  $+V_{SAT}$  because the voltage at inverting input is lower than at non-inverting input. The output waveform for a sinusoidal input signal is shown in Fig. 4.2. The schematic diagram of an inverting comparator and its output for a sinusoidal input are shown in Fig. 4.3 and Fig. 4.4. The diodes are used to protect the OPAMP from damage due to excessive input voltage. Because of these diodes, the difference in input voltage of the OPAMP is clamped either at +0.7 V or at -0.7 V. hence the diodes are called clamp

diodes. The resistances are used to limit the currents through the diodes. For OPAMPS with built in input protection the diodes can be removed.

 


Fig. 4.1. Circuit diagram of a non-inverting comparator

 


Fig. 4.2 Input and Output waveform of a non-inverting comparator

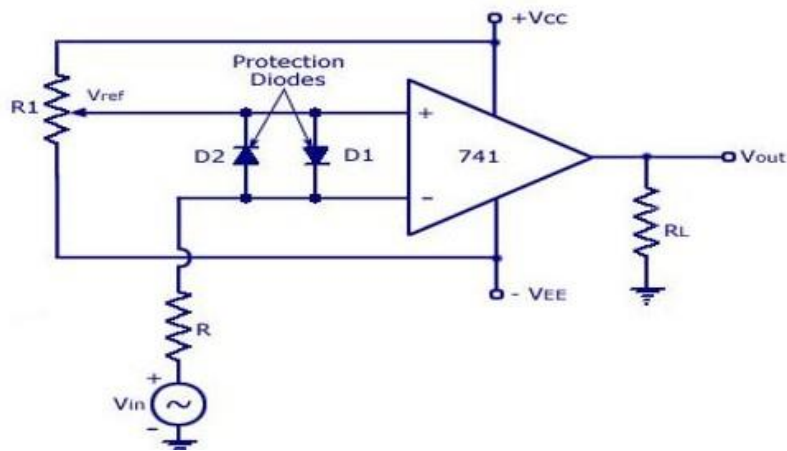


Fig. 4.3. Circuit diagram of an inverting comparator

 


Fig. 4.4. Input and Output waveform of an inverting comparator

## 2. Zero-crossing detector

In zero-crossing detector (or sine wave to square wave converter) the  $V_{ref}$  is set to 0 V. When the input voltage passes to zero in positive direction the output is driven in to negative saturation. Conversely, when the input voltage passes to zero in negative direction the output is driven in to positive saturation. Because of the noise at the OPAMPs input terminals, the output voltage may fluctuate between two saturation voltages  $+V_{SAT}$  and  $-V_{SAT}$ , detecting zero reference crossing for noise voltage as well as input voltage. Further if the input is a slowly varying waveform then input voltage will take more time to cross 0V.

Therefore output voltage may not switch quickly from one saturation voltage to another. These problems can be avoided with the use of regenerative or positive feedback

### 3. Schmitt Trigger

Schematic diagram of Schmitt trigger circuit is shown in Fig.4.5. The resistance  $R_{OM} = R_1 \parallel R_2$  is used to minimize the offset problem. The input voltage triggers (or changes the state of) the output every time it exceeds certain voltage levels, called upper threshold  $V_{ut}$  and lower threshold  $V_{lt}$ . The threshold voltages are obtained by using the voltage divider  $R_1$ - $R_2$ , where the voltage across  $R_1$  depends on the polarity of the output and is fed at the non-inverting input. Since the output voltage can be expressed as:

$$V_{ut} = \frac{R_1}{R_1 + R_2} V_{SAT}$$

And

$$V_{lt} = \frac{R_1}{R_1 + R_2} V_{SAT} \text{ respectively}$$

In  $v_{in} < v_{ut}$ , the output remains constant at  $+V_{sat}$ . When  $v_{in}$  is just greater than  $v_{ut}$ , the output regeneratively switches to  $-V_{SAT}$  and remains at this stage as long as  $v_{in} > v_{lt}$ . When  $v_{in} < v_{lt}$ , the output remains constant at  $+V_{SA}$ , till  $V_{in} > V_{ut}$ . These are shown in Fig.4.6. The figure shows that within  $v_{lt}$  and  $v_{ut}$  the output does not change state. The output changes its state only when  $v_{in} < V_{lt}$  or  $v_{in} > V_{ut}$ . Therefore, if the threshold voltages are made larger than the input noise, the Schmitt trigger circuit can be eliminate false output transition. The positive feedback, because of its regenerative action, makes the output to switch faster between  $+V_{SAT}$  or  $-V_{SAT}$ .

The comparator with positive feedback exhibit hysteresis, a dead-band condition, as shown. That is when the  $v_{in} > V_{ut}$  its output switches from  $+V_{SAT}$  or  $-V_{SAT}$  and reverts back to its original state  $+V_{SAT}$  when  $v_{in} < V_{lt}$ . The hysteresis voltage is the difference between  $v_{ut}$  and  $v_{lt}$  and is given by,

$$V_H = \frac{2R_1}{R_1 + R_2} V_{SAT}$$

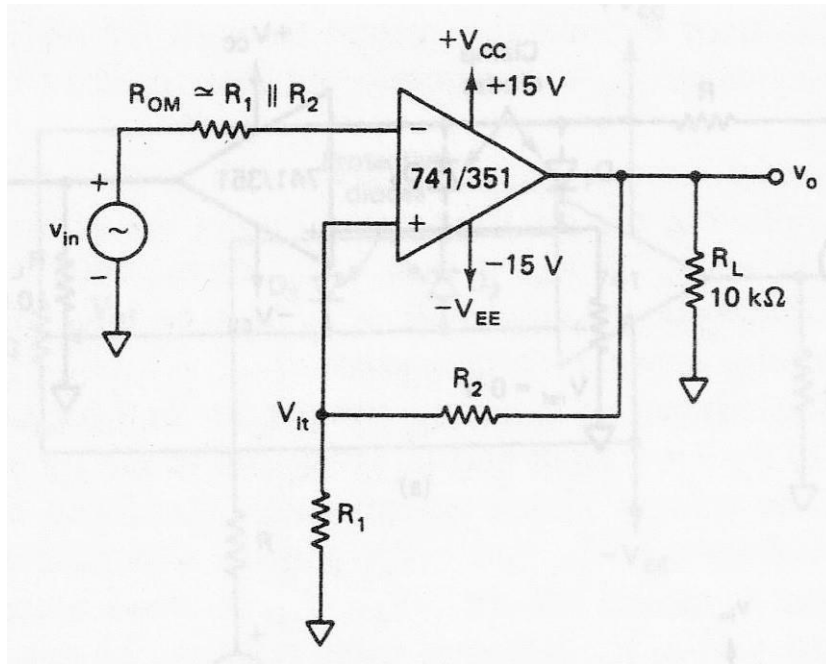


Fig. 4.5. Circuit diagram of a Schmitt Trigger.

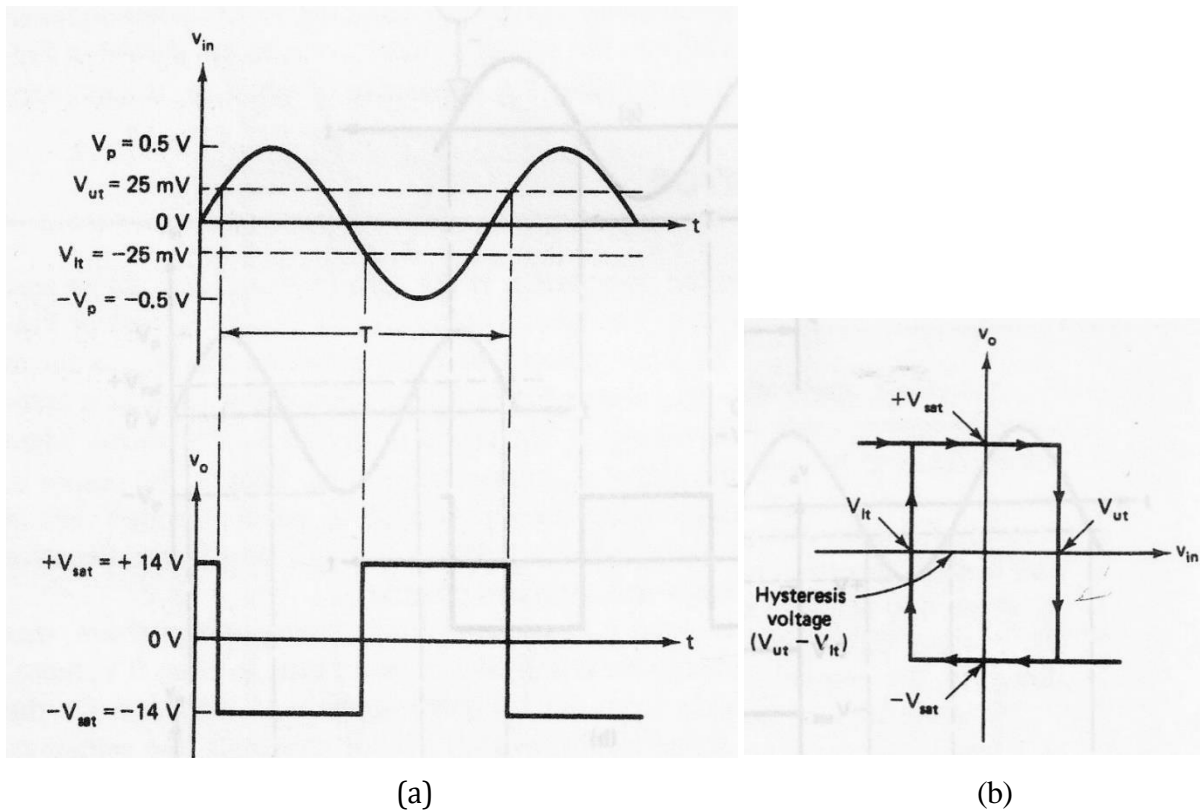


Fig. 4.6. (a) Input and Output waveform of a Schmitt Trigger and (b) Hysteresis in OPAMP Schmitt Trigger

**PROCEDURE:**

1. Connect the circuit as shown in the figure.
2. Setup the circuit on the breadboard / Multisim software and check the connections (for software simulation).
3. Connect the designated input to a sine wave signal generator with suitable peak to peak voltage at 1 – 2 kHz and remaining input with a suitable reference voltage (For comparators / zero-crossing detectors).
4. Plot the input waveform and output waveform on the same graph.
5. Plot hysteresis loop for the circuit (For Schmitt trigger circuit).

**OBSERVATION TABLE:**

**TABLE-1: FOR COMPARATOR / ZERO-CROSSING DETECTOR  
/SCHMITT TRIGGER**

Parameters	Input	Output
Voltage (Vp-p)		
Time period (ms)		

**TABLE-2: FOR SCHMITT TRIGGER**

Input Voltage	Output Voltage

**CONCLUSION:**

Non-inverting and inverting voltage comparators, zero crossing detector and Schmitt trigger circuits have been designed using op-amp and their output response have been studied.

**TYPICAL QUESTIONS:**

1. Why clamp diodes are used in comparator?
2. How to obtain high rate of accuracy in comparator?
3. How the op-amp comparator should be chosen to get higher speed of operation?
4. How to keep the output voltage swing of the op-amp comparator within specific limits?
5. What is the drawback in zero crossing detectors and state a method to overcome it.

6. Which circuit converts irregularly shaped waveform to regular shaped waveforms?
7. What happens if the threshold voltages are made higher than the noise voltages in Schmitt trigger?
8. In which configuration a dead band condition occurs in Schmitt trigger?
9. How to limit the output voltage swing only to positive direction?
10. What are the applications of Schmitt trigger?



## **EXPERIMENT – 05**

### GENERATION OF DIFFERENT WAVEFORMS USING OPAMP

#### (Part II)

**OBJECTIVE:**

After completion of this experiment, student will be able to design triangular wave and sine wave using OPAMP.

**APPARATUS AND COMPONENTS REQUIRED:**

1. Dual power supply +/- 15 V
2. DC power source
3. Oscilloscope
4. Bread board (for hardware) / Multisim Software (Software)
5. IC 741C
6. Resistors
7. Capacitors
8. Probes and connecting wires

**THEORY AND EXPLANATION****I. Triangular Wave Generator**

A triangular wave generator circuit is shown in Fig. 5.1. It consists of a comparator and an integrator. When the voltage at P goes slightly below or above 0 V, the output of the first OPAMP (A1) is at negative or positive saturation level, respectively. Let us assume the output of A1 is at positive saturation level  $+V_{sat}$ . This  $+V_{sat}$  is an input of the integrator A2. The output of A2, therefore, will be a negative-going ramp. Thus one end of the voltage divider  $R_2$ – $R_3$  is at the positive saturation level of A1 and the other is the negative-going ramp of A2. When the negative-going ramp attains a certain value  $-V_{Ramp}$ , point P is slightly below 0 V; hence output of A1 will switch from positive saturation to negative saturation  $-V_{sat}$ . This means that output of A2 will now stop going negatively and will begin to go positively. The output of A2 will continue to increase until it reaches  $+V_{Ramp}$ . At this time point P is slightly above 0 V; therefore output of A1 switched back to the positive saturation level  $+V_{sat}$ .

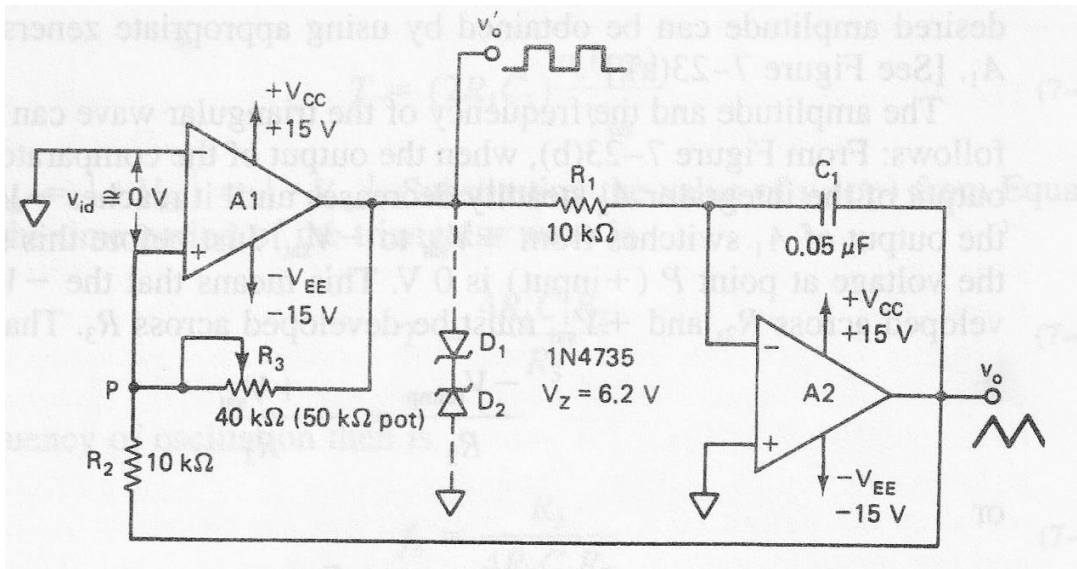


Fig. 5.1. Circuit diagram of a triangular wave generator

 


Fig. 5.2. Waveform at the output of the OPAMPs

The frequency of the square wave and triangular wave are same. The amplitude of the square wave is a function of dc supply voltages. However, a desired amplitude can be obtained by using appropriate Zeners at the output of A1, as shown. Just before the switching of output of A1 from  $+V_{sat}$  to  $-V_{sat}$ , the voltage at P is 0 V. Therefore we can write,

$$-\frac{V_{Ramp}}{R_2} = -\frac{+V_{sat}}{R_3},$$

$$\text{Or, } -V_{Ramp} = -\frac{R_2}{R_3}(+V_{sat}).$$

Similarly,

$$+V_{\text{Ramp}} = -\frac{R_2}{R_3}(-V_{\text{sat}})$$

Therefore peak-to-peak amplitude of the triangular wave is,

$$v_o(\text{pp}) = (+V_{\text{Ramp}}) - (-V_{\text{Ramp}}) = \left(-\frac{R_2}{R_3}(-V_{\text{sat}})\right) - \left(-\frac{R_2}{R_3}(+V_{\text{sat}})\right) = \frac{2R_2}{R_3}(+V_{\text{sat}})$$

The time taken by the output to swing from  $-V_{\text{Ramp}}$  to  $+V_{\text{Ramp}}$  is equal to the half of the time period  $T/2$ .

Therefore,

$$v_o(\text{pp}) = -\frac{1}{R_1 C_1} \int_0^{T/2} (-V_{\text{sat}}) dt = \frac{V_{\text{sat}}}{R_1 C_1} \frac{T}{2}$$

$$\text{Or, } T = 2R_1 C_1 \frac{v_o(\text{pp})}{V_{\text{sat}}} = \frac{2R_1 C_1}{V_{\text{sat}}} \frac{2R_2 V_{\text{sat}}}{R_3} = \frac{4R_1 C_1 R_2}{R_3}$$

$$\text{The frequency of oscillation is } f_o = \frac{R_3}{4R_1 C_1 R_2}$$

## II. RC- Phase Shift Oscillator

Schematic diagram of an OPAMP phase shift oscillator is shown in Fig. 5.3. In the circuit the OPAMP has been used in the inverting mode; therefore, any signal that appears at the inverting terminal is shifted by  $180^\circ$  at the output. At the resonance frequency  $f_o = 0.065/RC$ , the cascaded RC network provides another  $180^\circ$  phase shift; thus the total phase shift around the loop becomes  $360^\circ$  or  $0^\circ$ . At this frequency the gain of the amplifier must be at least 29, (i.e.,  $R_F = 29R_1$ ). To avoid loading effect we must set  $R_1 \geq 10R$ . A desired output can be obtained by using back-to-back Zener diode, as shown.

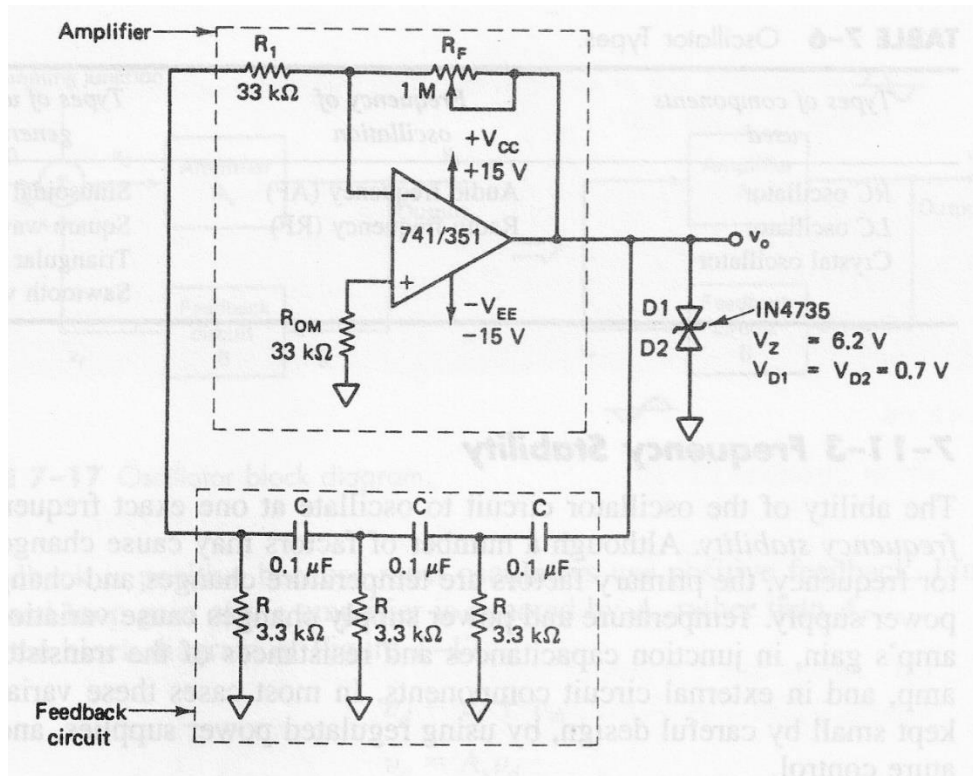


Fig. 5.3 Circuit diagram of a RC phase shift oscillator

 


Fig. 5.4. Output waveform of the RC phase shift oscillator

**PROCEDURE:**

1. Connect the circuit as shown in the Fig. 5.1 / Fig. 5.3 on the breadboard / Multisim software (for software simulation) and check the connections. You can initially neglect the diodes.
2. Connect the CRO at the outputs of the OPAMPs and ensure the correct waveforms at the respective outputs.

3. Plot the output waveforms of the OPAMPs.
4. Note the frequency / time periods the waveforms and compare them with the theoretical values.

**OBSERVATION TABLE:**

**TABLE-1: FOR SQUARE/TRIANGULAR WAVE GENERATOR.**

Parameters	Square Wave Output	Triangular Wave Output
Voltage Amplitude (Vp-p)		
Time period (ms)		

**TABLE-2: FOR RC PHASE SHIFT OSCILLATOR.**

Parameters	Sinusoidal Output
Voltage Amplitude (Vp-p)	
Time period (ms)	
Frequency ( $f_o$ )	
Comparison with theoretical frequency ( $f_o=0.065/RC$ ).	

**CONCLUSION:**

Different waveforms have been generated through designed waveform generator circuits. Triangular wave is generated by the triangular wave generator, whereas sinusoidal wave is generated through designed RC phase shift oscillator circuit using Op-Amp.

**TYPICAL QUESTIONS:**

1. What will happen if a fixed reference voltage, instead of ground, is connected at non-inverting terminal of integrator in Fig. 5.1?
2. How can the rise and fall time of triangular waveform be made unequal?
3. How the increase in the frequency of triangular wave will affect the magnitude of output waveform?
4. What is slew rate of a waveform generator circuit?
5. Why 3 RC network stages are used in phase shift oscillator?
6. What is Barkhausen criterion for oscillation?
7. What is an oscillator?
8. How can you control the frequency of the triangular wave in a triangular wave generator?
9. What is the function of the diodes in the triangular and RC-phase shift oscillator?
10. How do you calculate the values of R and C in a RC-phase shift oscillator?

#### **OTHER RELATED OPAMP CIRCUIT DESIGN:**

1. Design a triangular wave generator using a Schmitt-trigger and an integrator circuit.
2. Design a saw-tooth wave generator.
3. Design a Wien Bridge oscillator.
4. Design a quadrature Oscillator.

## **EXPERIMENT – 06**

DESIGN A COMMON EMITTER AMPLIFIER WITH PROPER Q-POINT SETTING AND STUDY THE FREQUENCY RESPONSE OF THE AMPLIFIER.

### **OBJECTIVE:**

After completing this experiment, the student will be able to design and set up a common emitter amplifier with proper Q-point setting and study its frequency response.

### **APPARATUS AND COMPONENTS REQUIRED:**

1. Regulated DC power supply.
2. Function generator
3. Oscilloscope
4. Breadboard (For Hardware) / Multisim Software (Software)
5. Resistor
6. Capacitor
7. Bipolar Junction Transistor

### **THEORY AND EXPLANATION:**

An amplifier is a device that amplifies the weak electric signals. One of the most common application of BJT is as an amplifier. For the BJT to act as an amplifier, it must be operated in the middle of the active region. A typical circuit diagram for a small signal common emitter (CE) amplifier is shown in Fig. 6.1. In this arrangement, potential divider bias has been used, which has the highest stability factor against variation of *beta*,  $\beta$ . The component values are such that it will drive the transistor into the active region. The emitter resistance further improves the stability and provides negative feedback to the base-emitter loop that reduces the overall gain of the transistor. A small signal to be amplified is connected to the base-emitter loop through coupling capacitor. The capacitors in the circuit block the dc signal therefore the operating point remains unchanged. The capacitor across the emitter resistance bypasses the ac signal and improves the amplifier's gain. Apart from the external capacitances, the BJT also have internal capacitances at the junctions. The presence of all these capacitance in the circuit makes the overall gain frequency-dependent.

 


Fig 6.1. Circuit diagram of common emitter amplifier

### **AMPLIFIER OPERATION**

Once the Q-point is fixed through DC bias, a sinusoidal signal is applied at the input through the coupling capacitor  $C_{C1}$ . During the positive half cycle of the input signal  $V_{BE}$  increases leading to an increased  $I$ . Therefore  $I_c$  increases by  $\beta$  times which reduces the output voltage,  $V_0$  as  $V_0 = V_{CC} - I_c R_c$ . Similarly, during the negative half cycle,  $I_c$  decreases which increases the output voltage. Thus the CE amplifier produces an amplified output with a phase reversal.

### **FREQUENCY RESPONSE CURVE**

An amplifier's performance is characterized by its frequency response curve that shows gain (dB) plotted against frequency. Fig 6.2 shows the typical frequency response characteristics of a CE amplifier. The frequency response of an amplifier can be divided into three frequency ranges. The curve is flat for the mid-range of frequencies. In the low-frequency range between 0 Hz and lower cutoff frequency, the external coupling and bypass capacitors decide the gain. However, at higher frequencies, the internal capacitances of the transistor play a significant role. The difference between lower and higher cutoff frequencies is called the bandwidth.



 


Fig. 6.2. Frequency response: Gain versus frequency plot

### **CIRCUIT DESIGN:**

*Calculating the resistances:*

The quiescent operating point or Q-point must be set at the centre position of load line for any small-signal amplifier to generate an amplified output with minimum distortion. Fig. 6.3 shows the voltage divider bias configuration. For the Q-point to be in the middle of the active region,  $V_{CE}$  should be 50% of  $V_{CC}$ .

To control the negative feedback,  $R_E$  should be sufficiently low. Ideally,  $R_C = 4R_E$ . Hence,  $V_{CE} = 0.5 V_{CC}$ ,  $V_E = 0.1 V_{CC}$ , and  $V_C = 0.4 V_{CC}$ .

 


Fig. 6.3. Voltage divider bias configuration

In the input section of voltage divider bias configuration, the equivalent resistance between base and ground is defined by  $R_i = (\beta + 1)R_E$ . The sensitivity to changes in  $\beta$  is relatively small if the value of  $R_{B2}$  is at least 10 times smaller than  $R_i$ , i.e,  $R_{B2} < 0.1 (\beta+1) R_E$ .

Applying KVL to the base –emitter loop of the transistor as shown in Fig.6.3,

$$V_B = V_{BE} + V_E$$

$$\text{or } \frac{V_{CC}R_{B2}}{R_{B1} + R_{B2}} = V_{BE} + V_E$$

$$\text{so that } R_{B1} = \frac{V_{CC}R_{B2}}{V_{BE} + V_E} - R_{B2}$$

**Calculating coupling capacitors  $C_{C1}$  and  $C_{C2}$ :**

Coupling capacitors  $C_{C1}$  and  $C_{C2}$  are used to separate the AC signals from the DC biasing voltage, so that the Q-point of the circuit remains undisturbed when input AC signal is applied.

The reactance  $X_{C1}$  of coupling capacitor  $C_{C1}$  should be less than the input resistance,  $R_{in}$  of the transistor.

$$X_{C1} \leq \frac{R_{in}}{10}$$

Here  $R_{in} = R_{B1} \parallel R_{B2} \parallel \beta r_e$

Where  $r_e (= \frac{26mV}{I_E})$  is the ac emitter resistance. The equivalent input ( $R_{in}$ ) and output ( $R_{out}$ ) resistance of the transistor are shown in Fig.6.4

 


Fig. 6.4. Circuit of CE amplifier showing input and output resistance.

For a lower cut-off frequency of  $f_L$  Hz:

$$C_{C1} = \frac{1}{2\pi f_L X_{C1}}$$

The reactance  $X_{C2}$  of coupling capacitor  $C_{C2}$  should be less than the output resistance,  $R_{out}$  of the transistor.

$$X_{C2} \leq \frac{R_{out}}{10}$$

Here,  $R_{out} = R_C$

$$\text{So, } C_{C2} = \frac{1}{2\pi f_L X_{C2}}$$

Calculating bypass capacitors  $C_E$ :

To bypass the lowest frequency,  $X_{CE}$  should be much less than or equal to the resistance  $R_E$ .

$$X_{CE} \leq \frac{R_E}{10}$$

$$\text{So, } C_E = \frac{1}{2\pi f_L X_{CE}}$$

## PROCEDURE:

1. Assume  $V_{CC}$ ,  $\beta$ , and  $R_E$  to calculate the value of rest of the components.
2. Set up the circuit on the breadboard / Multisim software and check the connections.
3. Apply suitable AC voltage levels at the input terminal. [Typical values 10-20 mV pp, Waveform: Sinusoidal]
4. Observe input and output on two channels of the oscilloscope simultaneously.
5. Note down the value of output voltage by varying the frequency from 10Hz to 10GHz.
6. Calculate the voltage gain (in dB) for each frequency.
7. Plot the frequency response curve, i.e., gain in dB versus frequency on a semilog graph-sheet.
8. Estimate the mid-frequency gain, the lower and higher cutoff frequencies, and hence the bandwidth.

## OBSERVATION TABLE:

To obtain the frequency response:

Fix the input amplitude and vary the frequency from 10Hz-10GHz and note down the output amplitude.

Sl. No.	Frequency (Hz)	Output voltage (Volt)	Gain ( $V_o/V_i$ )	Gain (dB)

### **OBSERVATIONS:**

Explain your result here.

### **CONCLUSION**

A CE amplifier with proper Q-point setting has been designed, and its frequency response has been studied. The upper and the lower 3dB cutoff frequencies are identified and marked on the response curve.

### **TYPICAL QUESTIONS:**

1. What are the advantages of common emitter amplifier circuit over other BJT amplifier circuits?
2. What are the applications of a common emitter amplifier?
3. Find the input impedance of a CE amplifier circuit.
4. Find the output impedance of a CE amplifier circuit.
5. Explain the significance of emitter resistance in the design of CE amplifier.
6. Explain the effect of a bypass capacitor on the passband gain of CE amplifier.
7. Explain the phase relationship between the input and output signals of CE amplifier.

### **OTHER RELATED BJT CIRCUIT DESIGN:**

1. Common base amplifier
2. Common collector amplifier
3. CE fixed base bias circuit
4. CE emitter-bias circuit
5. Collector to base bias circuit

## **EXPERIMENT – 07**

### **PERFORMANCE ANALYSIS (FREQUENCY RESPONSE) OF CASCADED AMPLIFIERS.**

#### **OBJECTIVE:**

After completing this experiment, the student will be able to design and set up a cascaded amplifier and study its frequency response.

#### **APPARATUS AND COMPONENTS REQUIRED:**

1. Regulated DC power supply.
2. Function generator
3. Oscilloscope
4. Breadboard (For Hardware) / Multisim Software (Software)
5. Resistor
6. Capacitor
7. Bipolar Junction Transistor

#### **THEORY AND EXPLANATION:**

An amplifier is a device that amplifies the weak electric signals. One of the most common application of BJT is as an amplifier. For the BJT to act as an amplifier, it must be operated in the middle of the active region.

#### **Multistage amplifier**

A single stage of amplification is often not enough for a particular application. For that, we have to use multiple stages of amplification for achieving the required voltage gain or power. This kind of amplifier is termed as a multistage amplifier analysis. In this amplifier, the first stage output is fed to the next stage input. Such type of connection is commonly known as cascading. RC coupled amplifier usually employed for voltage amplification. It consists of a coupling capacitor which is used to connect the output of the first stage to the base (i.e input) of the next stage. The resistors  $R_1$ ,  $R_2$ ,  $R_E$  forms the biasing and stabilizing network. The emitter bypass capacitor offers low resistance path to the signal. Without it, the voltage gain of the each stage would be lost. The coupling capacitor blocks DC and allows AC therefore this prevents the DC interference between the various stages and the shifting of operating

point. A typical circuit diagram for a multistage (cascaded) common emitter (CE) amplifier is shown in Fig. 6.1.

 


Fig 7.1. Circuit diagram of cascaded common emitter amplifier

**Operation:** When AC signal is applied to the base of the first transistor, it appears in the amplified form across its collector load  $R_c$ . the amplified signal developed across  $R_c$  is given to the next stage through coupling capacitor. The second stage does further amplification of the signal, in this way the cascaded stages amplify the signal and the overall gain is considerably increased and the bandwidth decreases. Capacitors  $C_1$  and  $C_3$  couple the input signal to transistors  $Q_1$  and  $Q_2$ , respectively.  $C_5$  is used for coupling the signal from  $Q_2$  to its load.  $R_1, R_2, R_{E1}$  and  $R_3, R_4, R_{E2}$  are used for biasing and stabilization of stage 1 and 2 of the amplifier.  $C_2$  and  $C_4$  provide low reactance paths to the signal through the emitter.

### Overall gain:

The total gain of a 2-stage amplifier is equal to the product of individual gain of each stage. Once the second stage is added, its input impedance acts as an additional load on the first stage thereby reducing the gain as compared to its no load gain. Thus the overall gain characteristics is affected due to this loading effect.

The loading of the second stage, i.e. input impedance of second stage,  $Z_{i2} = R_3 \parallel R_4 \parallel \beta r_{e2}$  Thus loaded gain of the first stage,  $A_{V1} = - (R_c \parallel Z_{i2}) / r_{e1}$

And, the unloaded gain of second stage,  $A_{V2} = - R_{C2} / r_{e2}$

The overall gain of the 2 stage amplifier is,  $A_{V1} = A_{V1} \times A_{V2}$

## FREQUENCY RESPONSE CURVE

An amplifier's performance is characterized by its frequency response curve that shows gain (dB) plotted against frequency. Fig 6.2 shows the typical frequency response characteristics of a CE amplifier. The frequency response of an amplifier can be divided into three frequency ranges. The curve is flat for the mid-range of frequencies. In the low-frequency range between 0 Hz and lower cut-off frequency, the external coupling and bypass capacitors decide the gain. However, at higher frequencies, the internal capacitances of the transistor play a significant role. The difference between lower and higher cut-off frequencies is called the bandwidth.

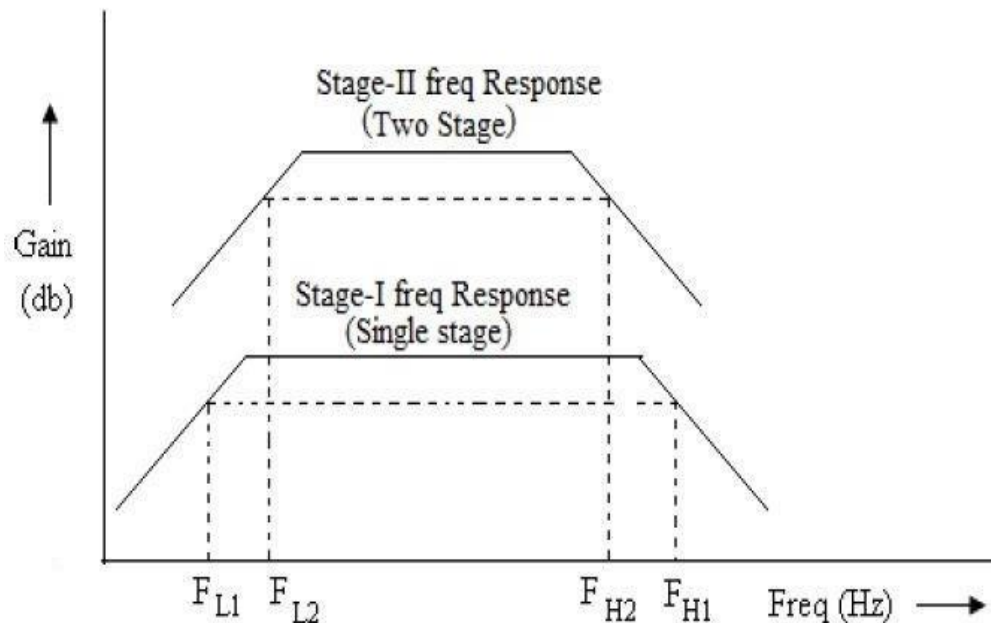


Fig. 7.2. Frequency response: Gain versus frequency plot

### CIRCUIT DESIGN:

#### **For individual stage:**

*Calculating the resistances:*

The quiescent operating point or Q-point must be set at the center position of load line for any small-signal amplifier to generate an amplified output with minimum distortion. Fig. 6.3 shows the voltage divider bias configuration. For the Q-point to be in the middle of the active region,  $V_{CE}$  should be 50% of  $V_{CC}$ .

To control the negative feedback,  $R_E$  should be sufficiently low. Ideally,  $R_C = 4R_E$ . Hence,  $V_{CE} = 0.5 V_{CC}$ ,  $V_E = 0.1 V_{CC}$ , and  $V_C = 0.4 V_{CC}$ .

For 2N222 transistor, Put  $\beta=100$ .

 


Fig. 7.3. Voltage divider bias configuration

In the input section of voltage divider bias configuration, the equivalent resistance between base and ground is defined by  $R_i = (\beta + 1)R_E$ . The sensitivity to changes in  $\beta$  is relatively small if the value of  $R_{B2}$  is at least 10 times smaller than  $R_i$ , i.e.,  $R_{B2} < 0.1(\beta + 1)R_E$ .

Applying KVL to the base-emitter loop of the transistor,

$$V_B = V_{BE} + V_E$$

$$\text{or } \frac{V_{CC}R_{B2}}{R_{B1} + R_{B2}} = V_{BE} + V_E$$

$$\text{so that } R_{B1} = \frac{V_{CC}R_{B2}}{V_{BE} + V_E} - R_{B2}$$

*Calculating coupling capacitors  $C_{C1}$  and  $C_{C2}$ :*

Coupling capacitors  $C_{C1}$  and  $C_{C2}$  are used to separate the AC signals from the DC biasing voltage, so that the Q-point of the circuit remains undisturbed when input AC signal is applied.

The reactance  $X_{C1}$  of coupling capacitor  $C_{C1}$  should be less than the input resistance,  $R_{in}$  of the transistor.

$$X_{C1} \leq \frac{R_{in}}{10}$$

Here  $R_{in} = R_{B1} \parallel R_{B2} \parallel \beta r_e$

Where  $r_e (= \frac{26mV}{I_E})$  is the ac emitter resistance. The equivalent input ( $R_{in}$ ) and output ( $R_{out}$ ) resistance of the transistor are shown in Fig.7.4



 


Fig.7.4 Circuit of CE amplifier showing input and output resistance.

For a lower cut-off frequency of  $f_L$  Hz:

$$C_{C1} = \frac{1}{2\pi f_L X_{C1}}$$

The reactance  $X_{C2}$  of coupling capacitor  $C_{C2}$  should be less than the output resistance,  $R_{out}$  of the transistor.

$$X_{C2} \leq \frac{R_{out}}{10}$$

Here,  $R_{out} = R_C$

$$\text{So, } C_{C2} = \frac{1}{2\pi f_L X_{C2}}$$

Calculating bypass capacitors  $C_E$ :

To bypass the lowest frequency,  $X_{CE}$  should be much less than or equal to the resistance  $R_E$ .

$$X_{CE} \leq \frac{R_E}{10}$$

$$\text{So, } C_E = \frac{1}{2\pi f_L X_{CE}}$$

## PROCEDURE:

1. Assume  $V_{CC}$ ,  $\beta$  ( $\approx 100$ , as transistor 2N2222 range between 50-200), and  $R_E$  to calculate the value of rest of the components.
2. Set up the circuit on the breadboard / Multisim software and check the connections.
3. Apply suitable AC voltage levels at the input terminal. [Typical values 10-20 mV pp, Waveform: Sinusoidal]
4. Observe input and output on two channels of the oscilloscope simultaneously.
5. Note down the value of output voltage by varying the frequency from 10Hz to 10GHz.
6. Calculate the voltage gain (in dB) for each frequency.
7. Plot the frequency response curve, i.e., gain in dB versus frequency on a semilog graph-sheet.
8. Estimate the mid-frequency gain, the lower and higher cutoff frequencies, and hence the bandwidth.

## OBSERVATION TABLE:

To obtain the frequency response:

Fix the input amplitude and vary the frequency from 10Hz-10GHz and note down the output amplitude.

Sl. No.	Frequency (Hz)	Output voltage (Volt)	Gain ( $V_0/V_i$ )	Gain (dB)

## OBSERVATIONS:

Explain your result here.

## CONCLUSION

A multistage CE amplifier with proper Q-point setting has been designed, and its frequency response has been studied. The upper and the lower 3dB cutoff frequencies are identified and marked on the response curve.

## EXPERIMENT – 08

### DRAIN AND TRANSFER CHARACTERISTIC OF FIELD EFFECT TRANSISTOR (FET)

#### OBJECTIVE:

To conduct experiment to study the transfer and drain characteristics of a JFET and determine its parameters.


#### APPARATUS AND COMPONENTS REQUIRED:

1. JFET(NPN) Q1A2N5454
2. Resistor (10K)
3. Variable power supply
4. Breadboard (For Hardware) / Multisim Software(Software)

#### THEORY AND EXPLANATION:
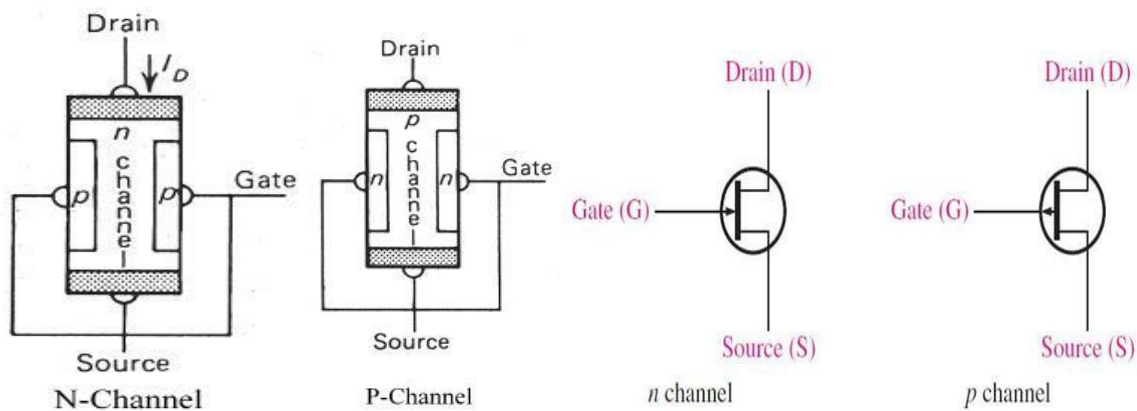
##### JFET

The JFET (Junction Field-Effect Transistor) is a type of FET that operates with a reverse-biased p-n junction to control current in a channel. Depending on their structure, JFETs fall into either of two categories, n channel or p channel. In n- channel JFET the drain is at the upper end, and the source is at the lower end. Two p-type regions are diffused in the n-type material to form a channel, and both p-type regions are connected to the gate lead. For simplicity, the gate lead is shown connected to only one of the p regions. The inverse of n-channel JFET is p-channel JFET.



**Transfer characteristics:** The range of  $V_{GS}$  values from zero to  $V_{GS}$  (off) controls the amount of drain current. For an n-channel JFET,  $V_{GS}$  (off) is negative, and for a p-channel JFET,  $V_{GS}$  (off) is positive. Because  $V_{GS}$  does control  $I_D$ , the relationship between these two quantities is very important. This curve is also known as a transconductance curve

**Drain saturation current  $I_{DSS}$ :** Maximum current flowing through JFET when gate to source voltage is zero.

**Pinch-off voltage  $V_P$ :** Gate to source voltage at which, drain current becomes zero.

**Transconductance  $g_m$ :** The forward transconductance (transfer conductance), is the change in drain current  $I_D$  for a given change in gate- to-source voltage  $V_{GS}$  with the drain-to-source voltage  $V_{DS}$  constant.


$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS} \text{ constant}}$$

**Drain characteristics:** The curve between drain current  $I_D$  and drain-source voltage  $V_{DS}$  of a JFET at constant gate-source voltage  $V_{GS}$  is known as drain characteristics of JFET.

**Drain dynamic resistance  $r_d$ :** The drain dynamic resistance is defined as the ratio of change in drain to source voltage  $V_{DS}$  to the change in drain current  $I_D$ , when gate to source voltage remain constant.



$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} \text{ constant}}$$

### **CIRCUIT DIAGRAM:**

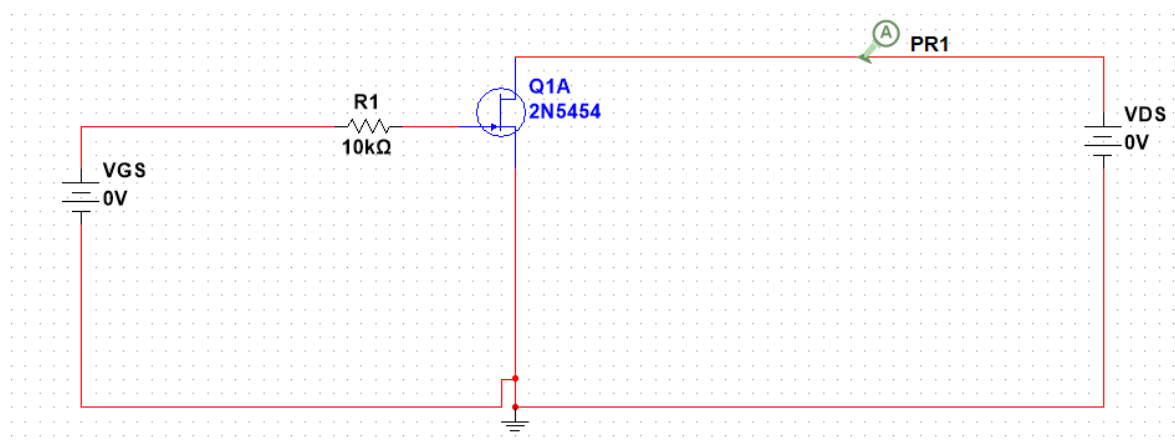

## Transfer Characteristics Observations:

Transfer Characteristics			
$V_{DS} = 15V$		$V_{DS} = 30V$	
$V_{GS}$ (V)	$I_D$ (mA)	$V_{GS}$ (V)	$I_D$ (mA)

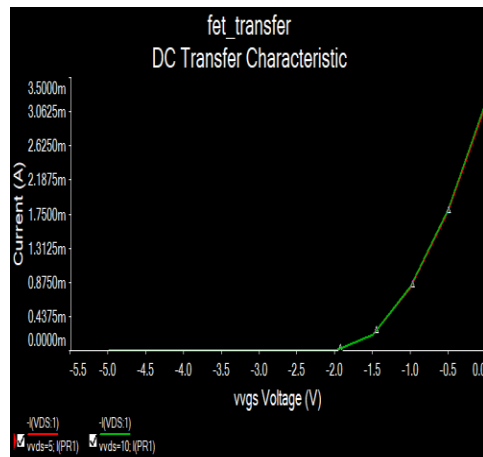 

## **CALCULATION**

Drain saturation current  $I_{DSS} =$

Pinch-off voltage  $V_P =$

$$\text{Transconductance } g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS} \text{ constant}}$$



## **PROCEDURE:**

1. Connect the circuit as per given diagram properly.
2. Set the voltage  $V_{DS}$  constant at 30 V.
3. Vary  $V_{GS}$  in the step of -5 V up to 0V in step 0.5 and note down value of drain current  $I_D$ . Tabulate all the readings.

4. Repeat the same procedure for  $V_{DS} = 15V$
5. Plot transfer characteristics  $V_{GS}$  vs  $I_D$  for constant  $V_{DS}$ .
6. Calculate  $I_{DSS}$ ,  $V_{GS}$  (off),  $g_m$  from the graphs and verify.

**Drain Characteristics Observations:**

<b>Drain Characteristics</b>					
$V_{GS} = 0V$		$V_{GS} = -1V$		$V_{GS} = -2V$	
$V_{DS}$ (V)	$I_D$ (mA)	$V_{DS}$ (V)	$I_D$ (mA)	$V_{DS}$ (V)	$I_D$ (mA)

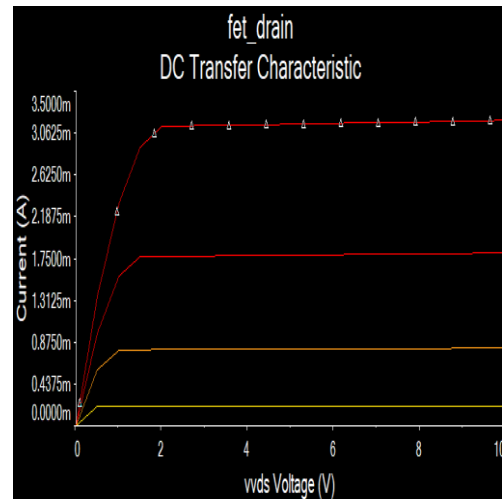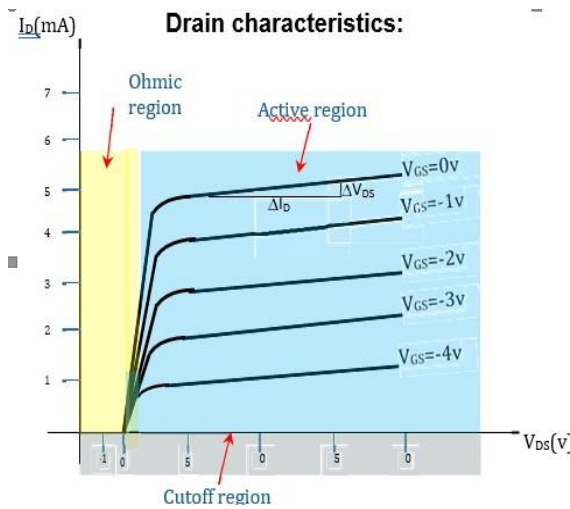

**Calculations:**

$$\text{Drain dynamic resistance } r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} \text{ constant}}$$

**Procedure:**

1. Connect the circuit as per given diagram properly.
2. Keep  $V_{GS} = 0V$  and vary  $V_{DS}$

3. Vary  $V_{DS}$  in step of -1V from 0 volts up to -3 volts and measure the drain current  $I_D$ . Tabulate all the readings.
4. Repeat the above procedure for  $V_{GS}$  as -1V, -2V, -3V etc.
5. Calculate  $r_d$  from the graphs and verify.

### **CONCLUSION:**

Drain and transfer characteristics have been obtained for N channel JFET also we have evaluated transconductance and drain resistance for the N channel JFET.

### **TYPICAL QUESTIONS:**

1. What are the advantages of FET?
2. Different between FET and BJT?
3. Explain different regions of V-I characteristics of FET?
4. What are the applications of FET?
5. What are the types of FET?
6. Draw the symbol of FET.
7. What are the disadvantages of FET?
8. What are the parameters of FET?

## **EXPERIMENT NO: 09**

### **REALIZATION OF CURRENT MIRROR CIRCUIT**

#### **OBJECTIVE:**

To conduct an experiment for the realization of current mirror circuit.

#### **APPARATUS AND COMPONENTS REQUIRED:**

1. Bread board
2. Regulated power supply
3. DSO
4. Transistor ( $Q_1$  and  $Q_2$ , any transistor with higher gain)
5. Resistors ( $R_2 = 4.7 \text{ K}$  to  $10 \text{ K ohm}$  and  $R_L = 0.100 \text{ K}$  to  $10 \text{ K ohm}$ )
6. Connecting wires
7. Multimeter
8. Multisim software

#### **THEORY:**

A current mirror is a circuit block which functions to produce a copy of the current flowing into or out of an input terminal by replicating the current in an output terminal. The simple two transistor implementation of the current mirror is based on the fundamental relationship that two equal size transistors at the same temperature with the same  $V_{GS}$  for a MOS or  $V_{BE}$  for a BJT have the same drain or collector current.


We would like a simple configuration where the active element, a single transistor, serves as the desired current-to-voltage converter. However, the transistor is a unidirectional device, where for the BJT the base emitter voltage controls the collector current.





A bipolar transistor can be driven by a voltage or by a current. The collector provides the output terminal of our simple current mirror: The output V to I converter stage of the simple current mirror is just a transistor acting as a non-linear (exponential for BJT) voltage-to-current converter.

 The final step is to connect the output of the input stage (the base emitter junction of  $Q_1$ ) to the input of the output stage (the base emitter junction of  $Q_2$ ) to build the basic BJT current mirror circuit.




If a voltage is applied to the BJT, the base-emitter junction acts as an input quantity and the collector current is taken as an output quantity. The transistor acts as exponential voltage-to-current converter and by applying a negative feedback (simply by joining the base and the collector), the transistor can be reversed. The simplest bipolar current mirror implements this idea. It consists of two cascaded transistor stages acting accordingly as reversed and direct voltage-to-current converters. The emitter of  $Q_1$  is connected to ground and the collector-base voltage is zero and the voltage drop across  $Q_1$  is  $V_{BE}$ . If  $Q_1$  and  $Q_2$  are matched, that is if they have same device properties and if the mirror output voltage is chosen so the collector-base voltage of  $Q_2$  is also zero, then the value of  $V_{BE}$  value set by  $Q_1$  results in an emitter current matched in  $Q_2$ . Because  $Q_1$  and  $Q_2$  are matched, their  $\beta$  values also agree, making the mirror output current the same as the collector current of  $Q_1$ .

The main specifications that characterize a current mirror circuit are:

1. Current transfer ratio
2. AC output resistance
3. Voltage drop

**CIRCUIT DIAGRAM:**

 

Current mirror circuit

**PROCEDURE:**

1. Make the connections as given in the circuit above.
2.  $I_{REF}$  is generated with respect to  $R_2 = R_{REF} = 4.7 \text{ K } \Omega$ ,  $V_{cc} = 12 \text{ volt}$ .
3.  $I_{C2}$  (collector current of  $Q_2$ ) was observed.
4. Load resistance,  $R_1$  is varied and the corresponding collector current is noted down.
5. Repeat the procedure 1 to 4 for  $R_2 = R_{REF} = 10 \text{ K } \Omega$ ,  $V_{cc} = 12 \text{ volt}$ .
6. The value of Load resistance ( $R_1$ ) for which  $I_{C1} = I_{C2}$ , the circuit can be designed which acts as current mirror circuit.

**OBSERVATION TABLE:**

$R_{ref} = R_2 = 4.7 \text{ k}\Omega$			$R_{ref} = R_2 = 10 \text{ k}\Omega$		
Load resistance( $R_1$ )	$I_{c1}(\text{mA})$	$I_{c2}(\text{mA})$	Load resistance( $R_1$ )	$I_{c1}(\text{mA})$	$I_{c2}(\text{mA})$
100 $\Omega$			100 $\Omega$		
200 $\Omega$			200 $\Omega$		
400 $\Omega$			400 $\Omega$		
600 $\Omega$			600 $\Omega$		
800 $\Omega$			800 $\Omega$		
1k $\Omega$			1k $\Omega$		
2k $\Omega$			2k $\Omega$		

3k $\Omega$			3k $\Omega$		
4k $\Omega$			4k $\Omega$		
5k $\Omega$			5k $\Omega$		
6k $\Omega$			6k $\Omega$		
7k $\Omega$			7k $\Omega$		
8k $\Omega$			8k $\Omega$		
9k $\Omega$			9k $\Omega$		
10k $\Omega$			10k $\Omega$		

### **CONCLUSION:**

The collector current  $I_{c2}$  was found approximately equal to the collector current  $I_{c1}$  at a particular value of  $R_1$ . It was verified for two different value of  $R_2 = R_{REF}=4.7 \text{ k}\Omega$  and  $10 \text{ k}\Omega$ .

### **PRECAUTIONS:**

1. Ensure that the polarity of the power supply is properly connected.
2. There should be no loose contacts at the junctions.

### **TYPICAL QUESTIONS:**

1. What is a current mirror in BJT?
2. How do you construct a current mirror using a BJT and MOSFET?
3. What is current sinking and current sourcing?
4. What are the applications of current mirror circuit?
5. What are the different techniques of designing current mirror circuits?
6. What is the difference between a practical and an ideal current mirror circuit?
7. What are the specifications of a proper current mirror circuit?
8. What are the limitations in real current mirror circuits?

### **OTHER RELATED CURRENT MIRROR CIRCUIT DESIGNS:**

1. Wilson current mirror
2. Widlar current mirror
3. Buffered feedback current mirror
4. Cascaded current mirror

## EXPERIMENT – 10

### DESIGN AND STUDY OF INPUT (DIFFERENTIAL PAIR) AND OUTPUT (DARLINGTON) STAGE OF OPAMP.

#### **OBJECTIVE:**


To conduct experiment to study the differential pair amplifier connected at input side and Darlington stage at output side of internal structure of OPAMP.

#### **APPARATUS AND COMPONENTS REQUIRED:**

1. Bread Board
2. Regulated power supply
3. Digital storage oscilloscope
4. Function generator
5. NPN Transistor BC547A & BC107BP
6. Resistor (4.7K $\Omega$ , 10 K $\Omega$ , 1M $\Omega$ , 100K $\Omega$ )
7. Capacitor (two 10 $\mu$ F)
8. Connecting wires
9. Multimeter

#### **THEORY AND EXPLANATION:**

The internal structure of OPAMP is shown in figure 1.

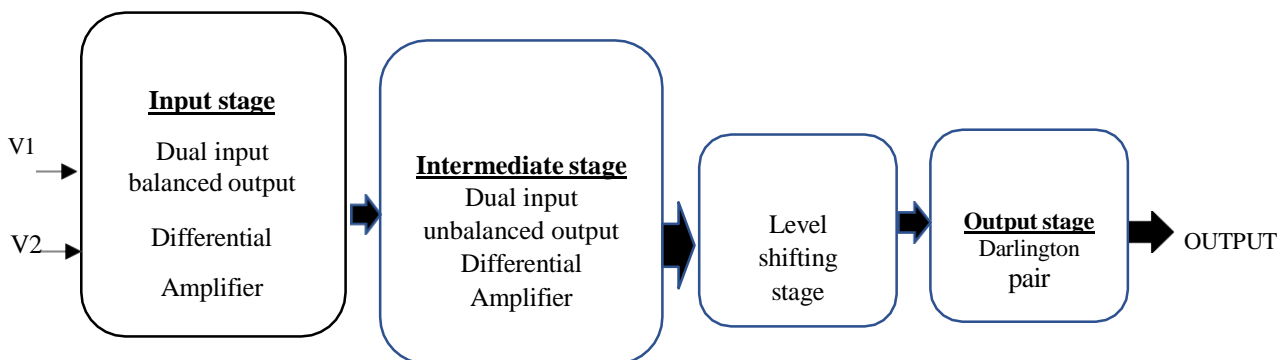

**Fig.10.1 Block diagram of internal structure of OPAMP.**

## 1. Differential Amplifier

A differential amplifier is most widely used circuit building block in analog integrated circuit. For instance, input stage of every op-amp amplifier is a differential amplifier. BJT differential amplifier is the basis of a very high-speed logic circuit family called emitter-coupled logic (ECL). The differential amplifier as the name suggests amplifies the difference between two input signal  $v_{in1}$  and  $v_{in2}$ . BJT differential pair configuration consists of two matched transistors Q1 and Q2, whose emitters are formed together and biased by a constant current source I. Latter is usually implemented by a transistor circuit. The two collectors may be connected to another transistor rather than to resistive loads. It is essential though that the collector circuits be such that Q1 and Q2 can never enter saturation.

Gain of differential amplifier is given by:

$$A_d = \frac{V_o}{V_d}$$

$$\text{where, } V_d = V_{in1} - V_{in2}$$

### CIRCUIT DIAGRAM:

 


Fig.10.2 Differential amplifier using transistor where ( $R_{C1}=R_{C2}=4.7K\Omega$  &  $R_E=10K\Omega$ ,  $V_{CC}=12V$  and  $V_{EE}=-12V$ )

### PROCEDURE:

1. Connect the circuit as per diagram on the bread-board.
2. Connect 12V power supply.
3. Connect the  $v_{in1}$  and  $v_{in2}$  voltages to the circuit.

4. Measure the output voltage from oscilloscope.
5. Find the gain using output voltage and difference of input voltage.

**OBSERVATION:**

SL. No.	V <sub>in1</sub>	V <sub>in2</sub>	V <sub>out</sub>	Ad (Gain)
1.	10mV	20mV		
2.	20mV	5mV		
3.	5mV	8mV		

**2. DARLINGTON PAIR**

The Darlington transistor (often called a Darlington pair) is a compound structure consisting of two bipolar transistors (either integrated or separated devices) connected in such a way that the current amplified by the first transistor is amplified further by the second one. This configuration gives a much higher common/ emitter current gain than each transistor taken separately. In the Darlington pairs, transistor collectors are tied together and the emitter of the first is directly coupled to the base of the second transistor. The total gain, which is often 1000 or more, is the product of the gain of the individual transistors. For large currents it is standard and good procedure to use a Darlington pair of transistors, rather than a single one, which effectively acts like a single transistor with  $\beta$  that is the two  $\beta$ s of the individual transistors.

The Darlington pair has an overall current gain of:

$$\beta_d = \beta_1\beta_2 \tag{10.1}$$

where,  $\beta_d = \frac{I_C}{I_B}$

The key advantage of the Darlington configuration is that the total current gain of the circuit equals the product of the current gain of two devices since its current gain is much higher. It combines two bipolar transistors in a single device; hence they require lesser space than configurations that use two discrete transistors. Darlington connection can have high input impedance and can produce very large outputs current. The disadvantage is the larger saturation voltage compared to single transistor configurations. Darlington transistors also have a higher base emitter voltage which is sum of both base emitter voltage.

## CIRCUIT DIAGRAM:

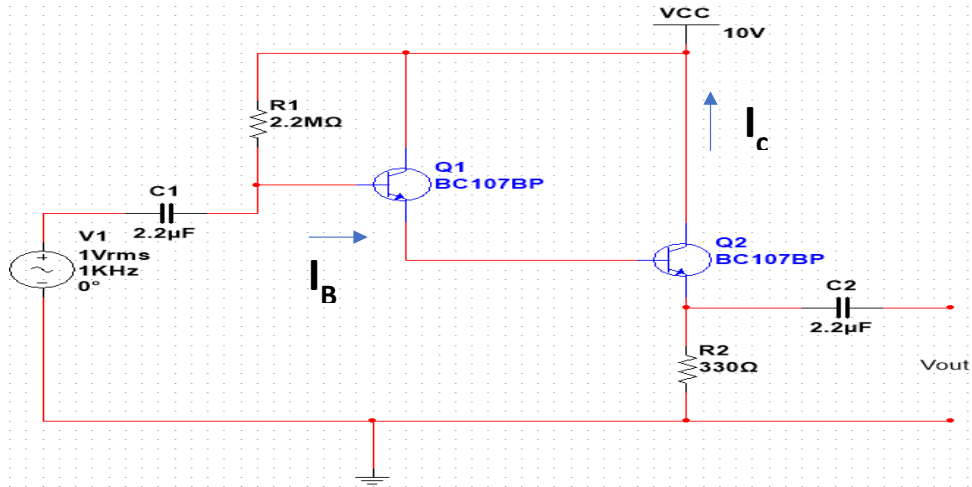


Fig. 10.2: Circuit diagram of Darlington pair.

## PROCEDURE:

1. Connect the circuit as shown in the figure 2.
2. Note down input current  $I_B$  and output current  $I_C$  for different value of source voltage.
3. Check  $\beta_1$ ,  $\beta_2$  and the overall current gain relationship for Darlington pair ( $\beta_d = \beta_1\beta_2$ ) is valid for different value of source voltage.

## OBSERVATION:

SL. No.	V1	$\beta_1$	$\beta_2$	$\beta_d$
1.	1V			
2.	2V			
3.	5V			

## PRECAUTIONS:

1. The breadboard should be handled carefully.
2. All connections should be neat and tight.

